



Introduction to Electronics **Laboratory**

EXPERIMENT-11

**Differential Amplifiers
using MOSFETS**

Shorya Sharma
19EE01017

OBJECTIVES

- DC Analysis of the differential amplifier.
- AC Analysis with same R_1 and R_2 .
- AC Analysis without same R_1 and R_2 .

THEORY


The differential amplifier is a circuit which amplifies the difference between signals applied to the inputs. The input signals to a differential amplifier in general contains two components named as common mode and difference mode signals. The common mode is average of two input signals and the difference mode is the difference between the two inputs. In ideal case the differential amplifier should affect the difference mode signal only. However, the common mode signal is also amplified to some extent. The Common mode rejection ratio(CMRR) is defined as the ratio of the difference signal voltage gain to the common mode signal voltage gain. For a good quality differential amplifier the CMRR should be very large.

In DC-Analysis we will check the three mosfets to be in saturation. The condition for saturation is voltage between gate and drain must be less than the threshold voltage. As per the mosfet it is given that it has the threshold voltage of 0.8V and VDD of 5V.


In AC-Analysis the difference mode gain(A_d) is $(V_{out1} - V_{out2}) / (V_{in1} - V_{in2})$ which is the ratio of difference in output voltage to the difference in input voltage which will be a large value and common mode gain(A_c) is $(V_{out1} - V_{out2}) / ((V_{in1} + V_{in2}) / 2)$ the ratio of difference between output voltages to the average of input voltages. Using these we will find out the CMRR. The ratio of A_d and A_c .

CIRCUIT DIAGRAMS


CASE-1: DC-ANALYSIS

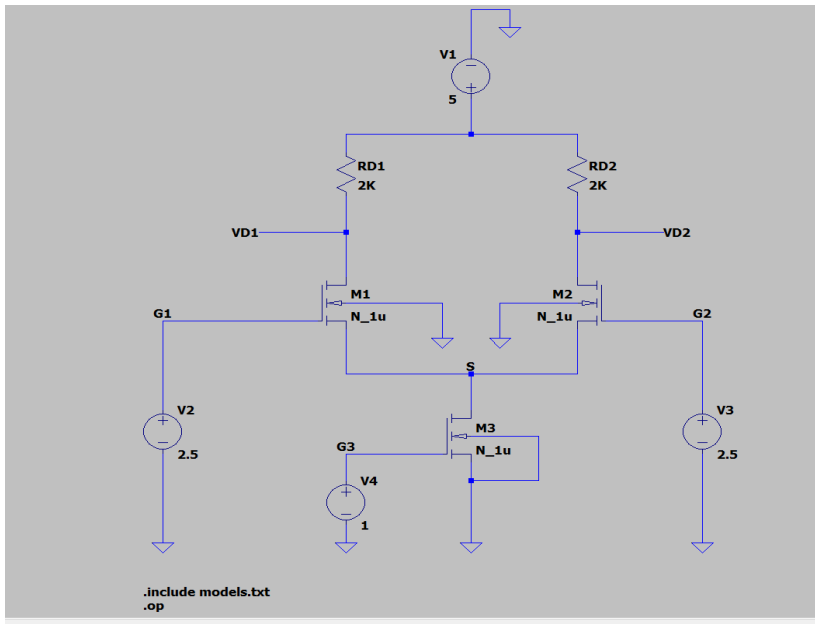

CASE-2: AC-ANALYSIS

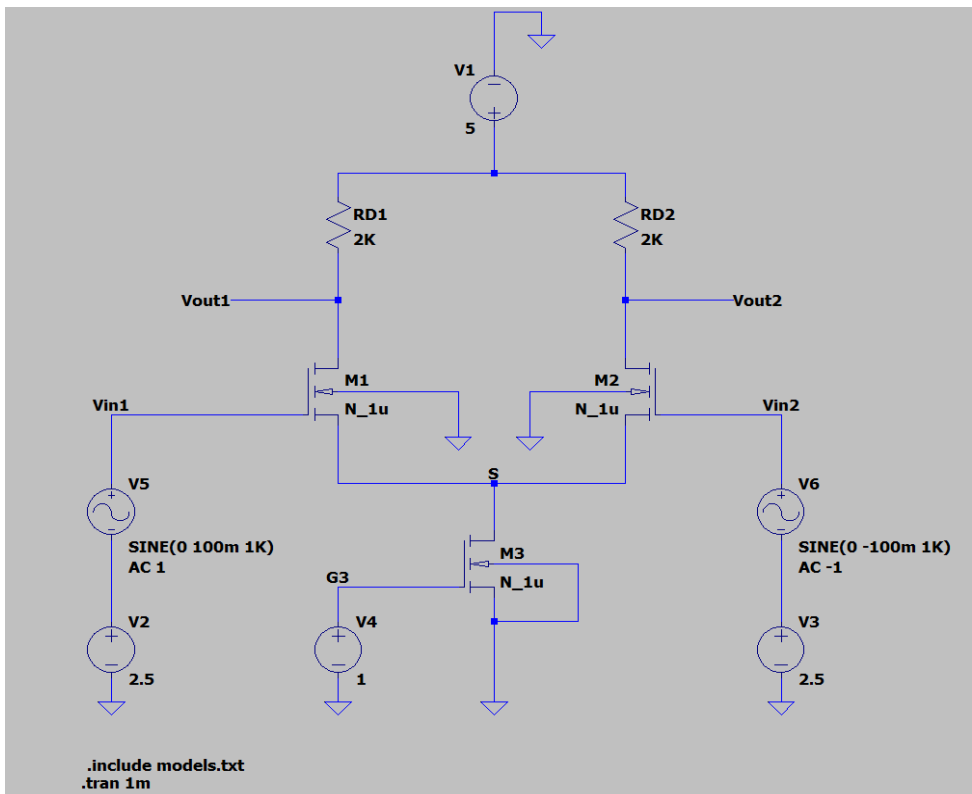

CASE-3: R1 and R2 are changed

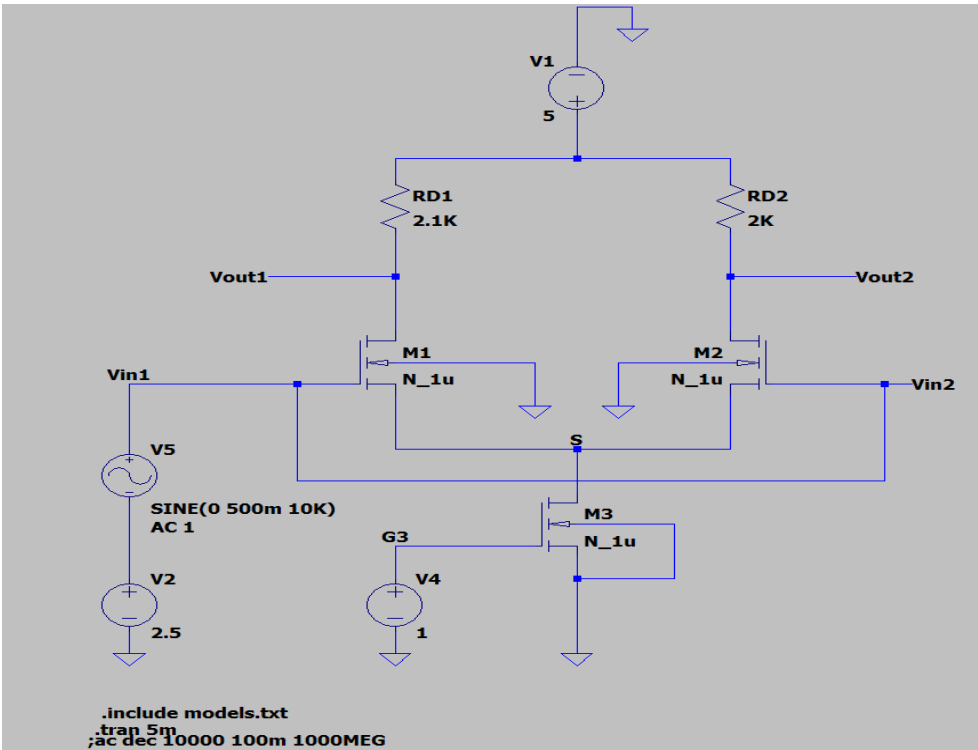

GRAPHS AND CALCULATIONS

DC-ANALYSIS

```
--- Operating Point ---  
V(vd1) :      4.0095      voltage  
V(vin1) :      2.5       voltage  
V(n001) :      1.08999    voltage  
V(vd2) :      4.0095    voltage  
V(vin2) :      2.5       voltage  
V(vgs3) :      1.5       voltage  
V(vdd) :      5         voltage  
Id(M3) :      0.000990462 device_current  
Ig(M3) :      0         device_current  
Ib(M3) :      -1.09999e-012 device_current  
Is(M3) :      -0.000990462 device_current  
Id(M2) :      0.000495177 device_current  
Ig(M2) :      0         device_current  
Ib(M2) :      -5.11949e-012 device_current  
Is(M2) :      -0.000495177 device_current  
Id(M1) :      0.000495177 device_current  
Ig(M1) :      0         device_current  
Ib(M1) :      -5.11949e-012 device_current  
Is(M1) :      -0.000495177 device_current  
I(R2) :      0.000495248 device_current  
I(R1) :      0.000495248 device_current  
I(V4) :      0         device_current  
I(V3) :      0         device_current  
I(V2) :      0         device_current  
I(V1) :      -0.000990496 device_current
```

For M1; $V_{gd} = V_g - V_d = 2.5 - 4.0095 = -1.5095V$


For M2; $V_{gd} = V_g - V_d = 2.5 - 4.0095 = -1.5095V$

For M3; $V_{gd} = V_g - V_d = 1.5 - 1.0899 = 0.41001V$

AC-ANALYSIS

CASE-1


Ad

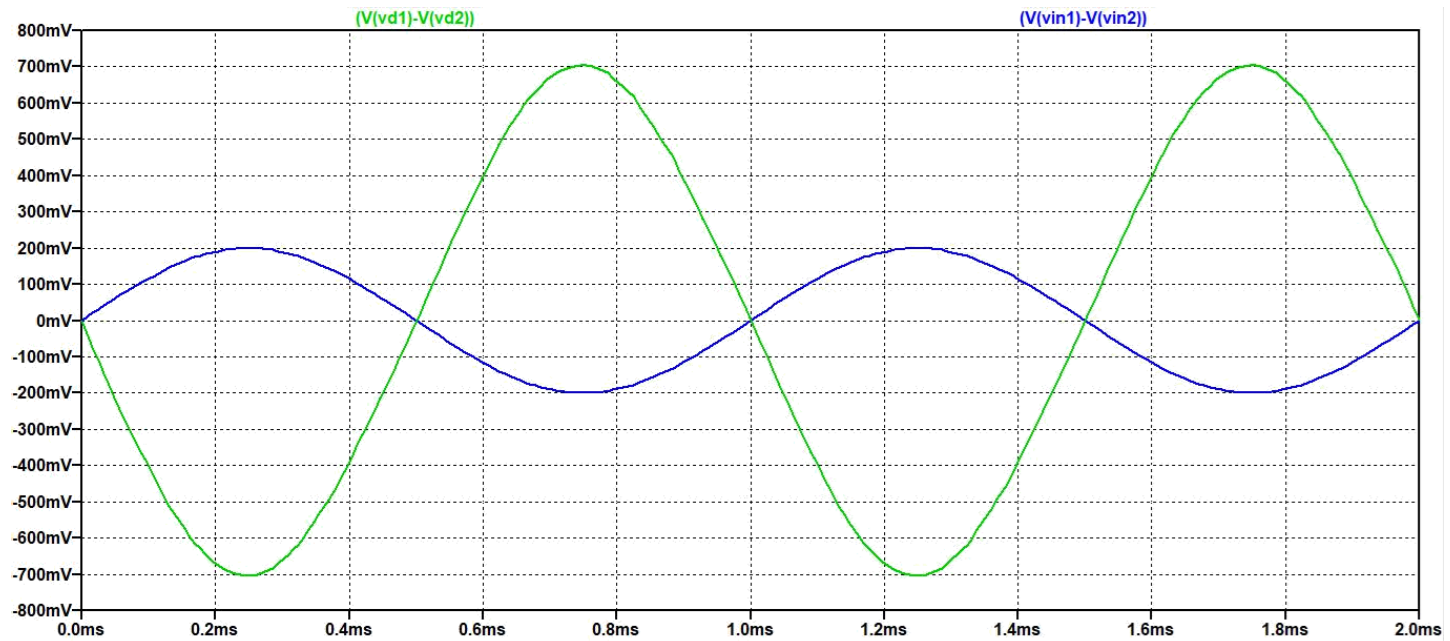

$$A_d = (V_{out1}-V_{out2}) / (V_{in1}-V_{in2}) = -700\text{mV} / 200\text{mV} = -3.5 \text{ V/V}$$

(as they are in out of phase negative sign occurs)

Ac

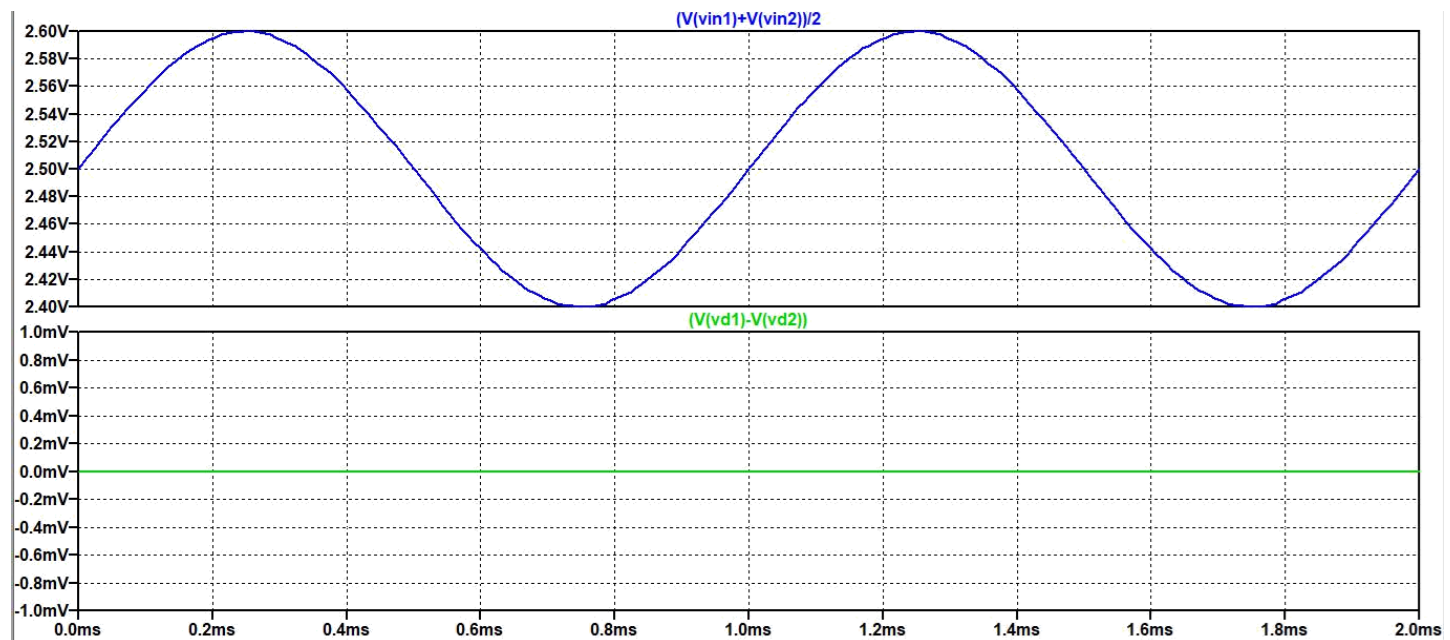


$$A_c = (V_{out1} - V_{out2}) / (0.5 * (V_{in1} + V_{in2})) = 0\text{mV} / 500\text{mV} = 0\text{V/V}.$$

(negative shows they are in out of phase)

$$\text{CMRR} = A_d / A_c = -3.5 / 0 = -\text{infinite}.$$

CASE-2


Ad

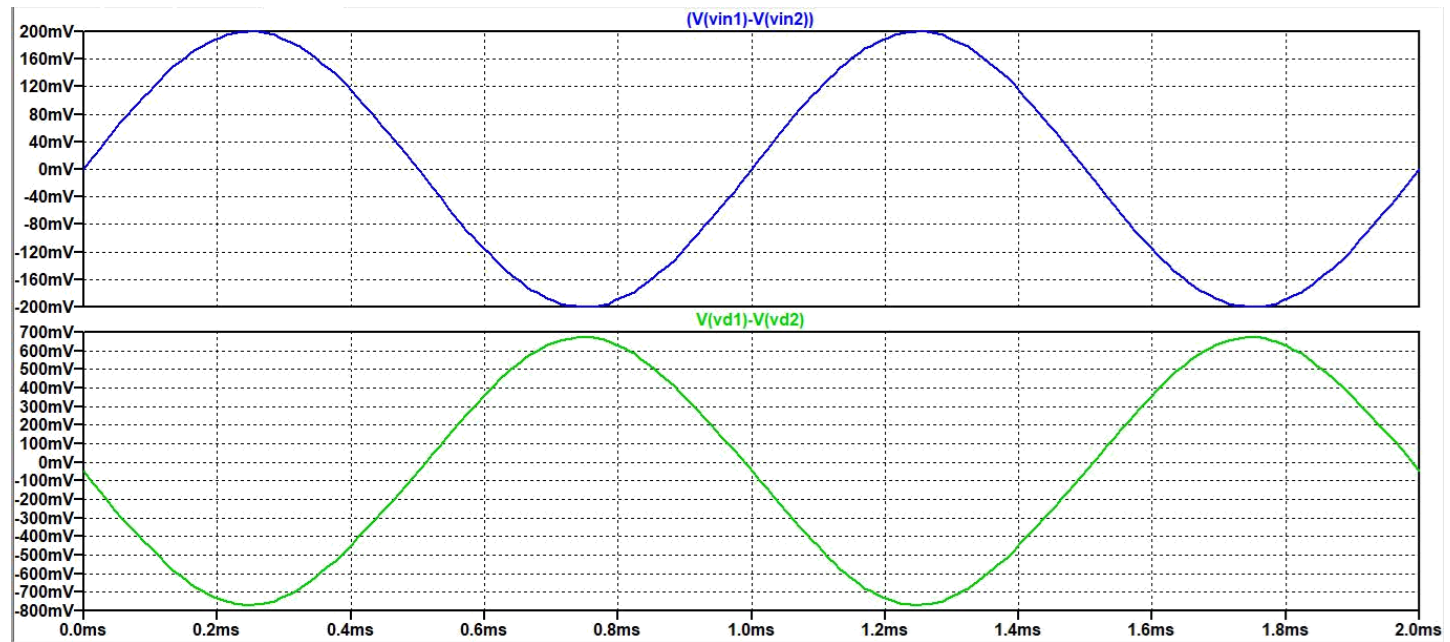

$$A_d = (V_{out1}-V_{out2}) / (V_{in1}-V_{in2}) = -721\text{mV}/200\text{mV} = -3.605 \text{ V/V}$$

(as they are in out of phase negative sign occurs)

Ac

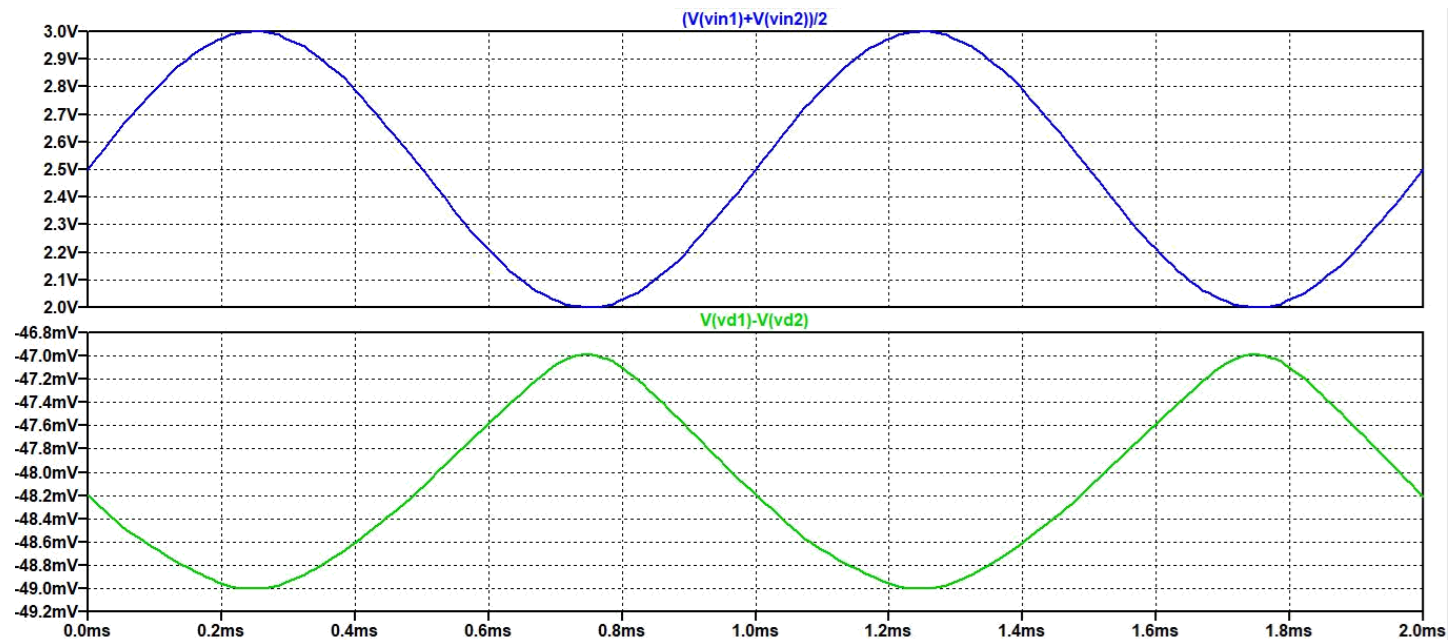

$$A_c = (V_{out1}-V_{out2})/(0.5*(V_{in1}+V_{in2})) = -1mV/100mV = -0.01$$

V/V. (negative shows they are in out of phase) $CMRR = A_d/A_c = -$

$$3.605/-0.01 = 360.5.$$

$$CMRR(dB) = 20\log(|CMRR|) = 51.138dB.$$

RESULTS

DC-ANALYSIS

For M1; $V_{gd} = -1.5095V < 0.8 = V_t$

For M2; $V_{gd} = -1.5095V < 0.8 = V_t$

For M3; $V_{gd} = 0.41001V < 0.8 = V_t$

It shows that all mosfets are in saturation.

AC-ANALYSIS

Case-1

$A_d = -3.5V/V$

$A_c = \text{infinite.}$

Case-2

$A_d = -3.605V/V$

$A_c = -0.01 V/V.$

We can observe that the A_d is larger value than A_c .

$CMRR = 360.5.$

$CMRR(\text{in dB}) = 51.138\text{dB}.$

DISCUSSION

In DC-Analysis we first simulated DC operating points to get the voltages at every node and found the values of V_{gd} for each mosfet. From this we got to know that for $R1$ and $R2$ as $2K\Omega$ the three mosfets are in saturation that is $V_{gd} < V_t$. V_t is threshold voltage of the mosfet.

Then done the AC-Analysis to find the A_d -difference mode gain for this we gave inputs as out of phase to each other, then to find the A_c -common mode gain we gave same inputs otherwise also can be said as we shorted both inputs. Then found A_d and A_c further CMRR got as infinite as A_c is zero in that case. This shows it has no common mode.

So now increased the $R1$ by small increment made it $2.1k\Omega$ to get some value of the A_c , it is a very small value and now the CMRR is a large value that can be compared to the A_d .this is the second case.

CONCLUSION

We understood the working of differential amplifier, also it is the basic part of op-amp and many components. Without the differential amplifier the world of electrical components used for amplifying would be nothing. This amplifies the input signals difference and mainly useful for getting rid of the noise produced. The A_c should be as small as possible for having less noise.
