



# **Power Electronics Laboratory** **(EE3P004)**

## **EXPERIMENT-6**

**To study the operation of cyclo converter**  
**with R-L Load**

***Shorya Sharma***  
***19EE01017***


## AIM OF THE EXPERIMENT:

To study the operation of cyclo converter with R-L Load


## APPARATUS REQUIRED:

- Cyclo Converter module (PEC14M14CY)
- Oscilloscope
- Patch Chord

## CIRCUIT DIAGRAM:

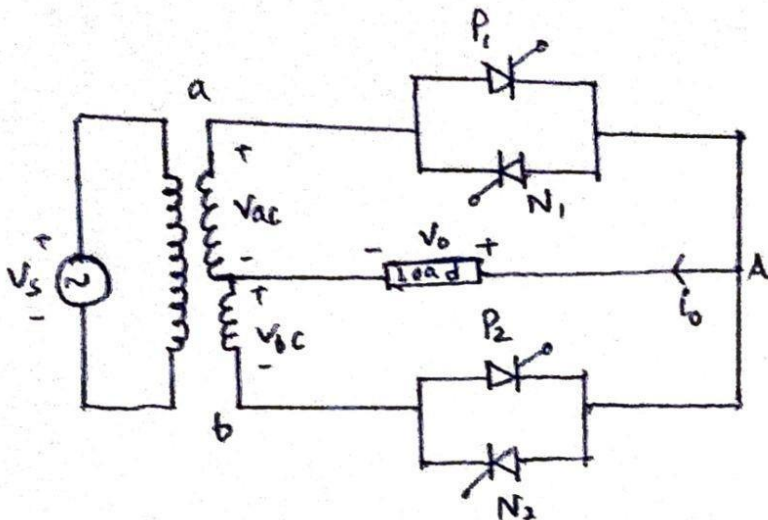


## CIRCUIT SCHEMATIC:

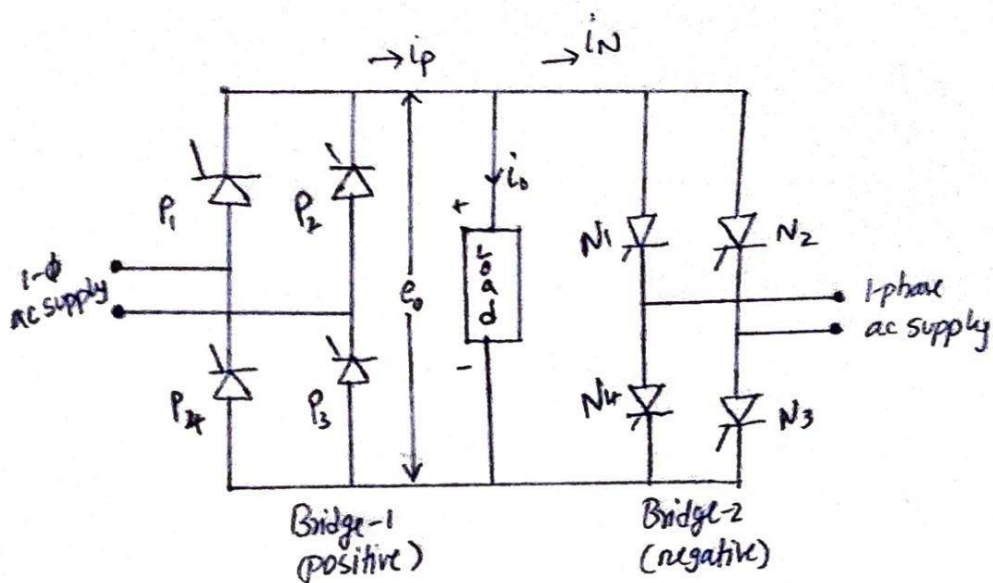

**OBSERVATION:**

Frequency Division	Firing angle ( $\alpha$ )	$V_{p,p}$ (V)	$V_{rms}$ (V)
1	0	69.2	22.4
	45	68.4	21.8
	90	68.8	15.4
2	0	69.2	24.4
	45	61.6	21.9
	90	56.8	16.4
3	0	69.2	25.6
	45	57.2	21.9
	90	51.6	15.5
4	0	69.6	24.5
	45	69.2	22.9
	90	52.8	16.1

## Waveform:

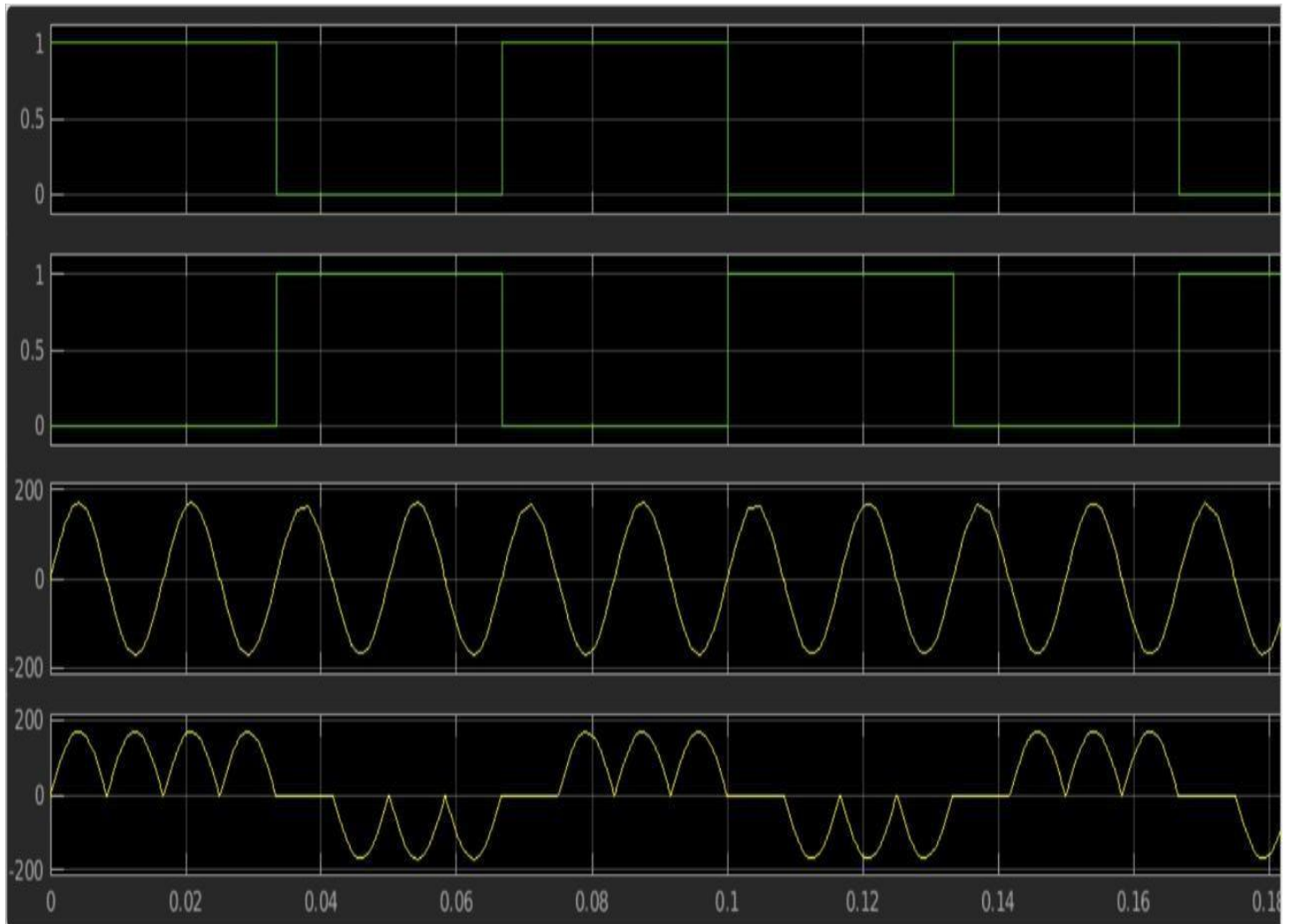

## CONCLUSION

We have noted the readings of voltage across the load at different frequency divisions and firing angles appropriately. We have also measured the voltage  $V_{p-p}$  accordingly. Hence our aim to study the operation of cyclo converter with R-L Load is accomplished successfully.