

INDIAN INSTITUTE OF TECHNOLOGY BHUBANESWAR



Introduction to Electronics Laboratory

School of Electrical Sciences

Name: Shorya Sharma

Roll Number: 19EE01017

AIM:-


- To analyze Forward characteristics of all Diodes.
- To analyze Reverse characteristics of 4.7V Zener Diode.
- Drawing some conclusion from results

Part 1

Analyzing Forward characteristics of all Diodes


- Silicon Diode

Circuit Diagram

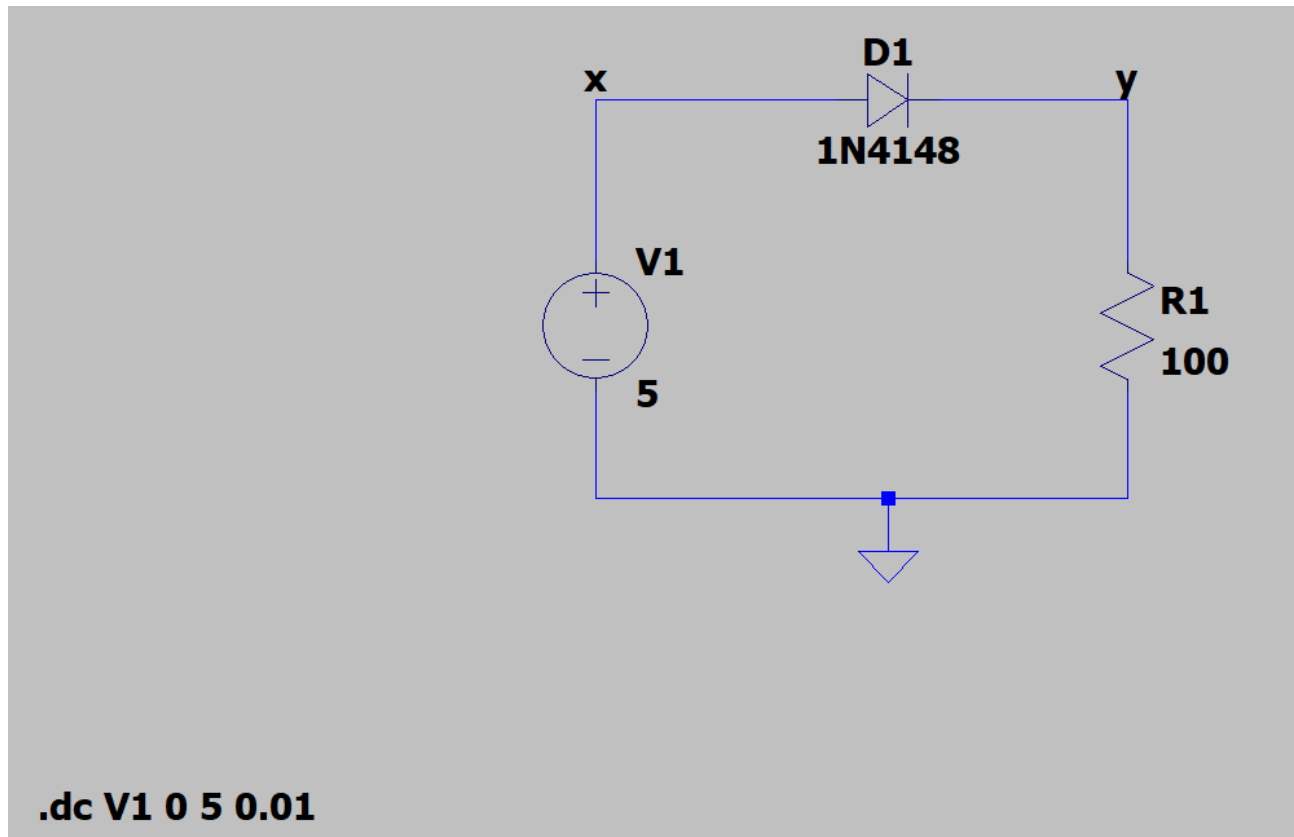

The model of Silicon diode, I used here is 1N4148 which has breakdown voltage of 75volts.

Output from LTspice simulation

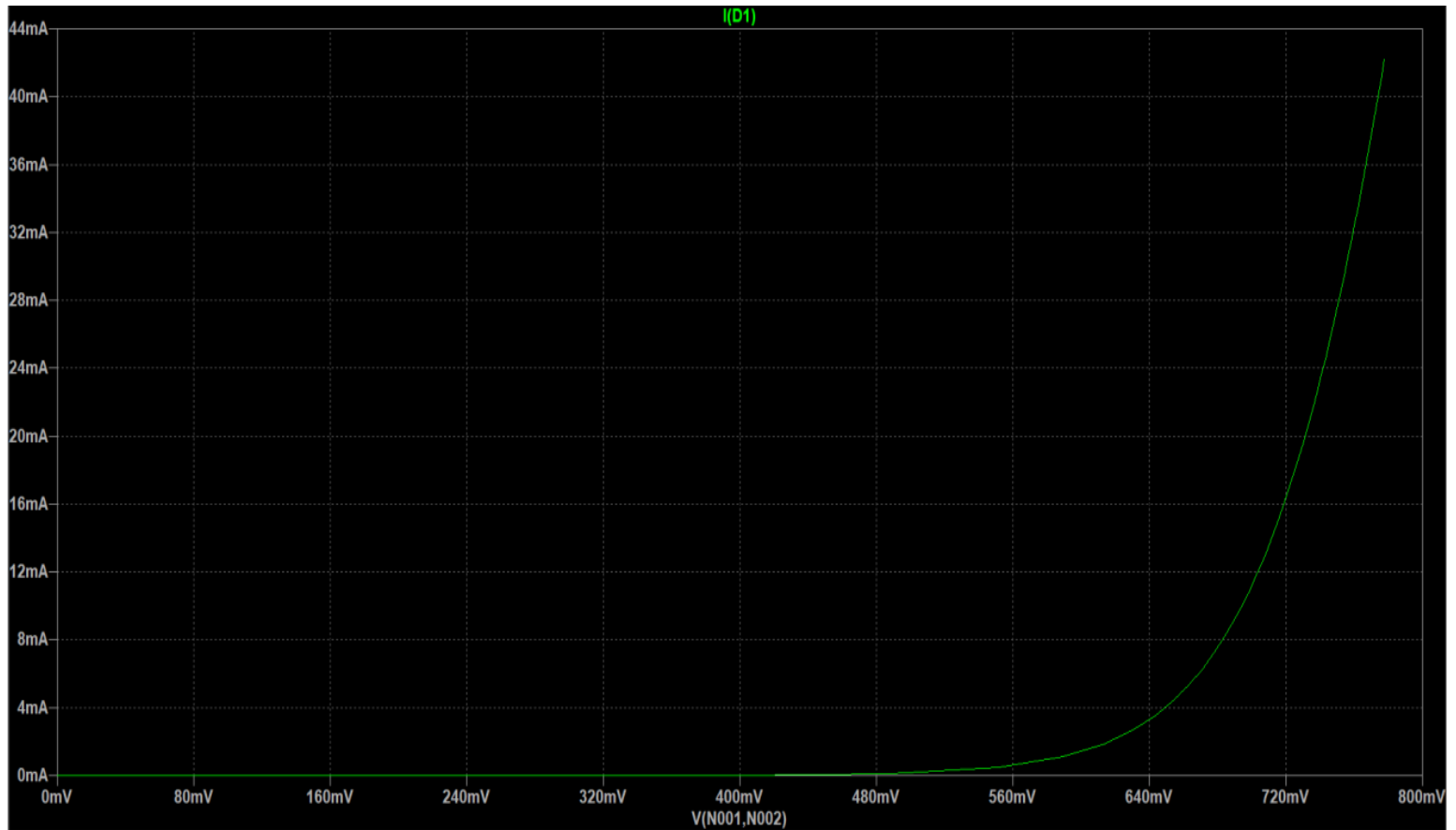


Observation Table:

| Characteristics of silicon diode | | | | | | |
|------------------------------------|--|--|--|----------------------------------|--|--|
| | | | | | | |
| | | | | | | |
| Voltage across diode V_D (volts) | | | | Diode Forward current I_D (mA) | | |
| 0 | | | | 0 | | |
| 0.24 | | | | 0.00087 | | |
| 0.4 | | | | 0.0184 | | |
| 0.48 | | | | 0.11 | | |
| 0.56 | | | | 0.622 | | |
| 0.64 | | | | 3.3 | | |
| 0.72 | | | | 16.33 | | |
| 0.751 | | | | 28.06 | | |
| 0.774 | | | | 40 | | |


- Zener Diode

Circuit Diagram

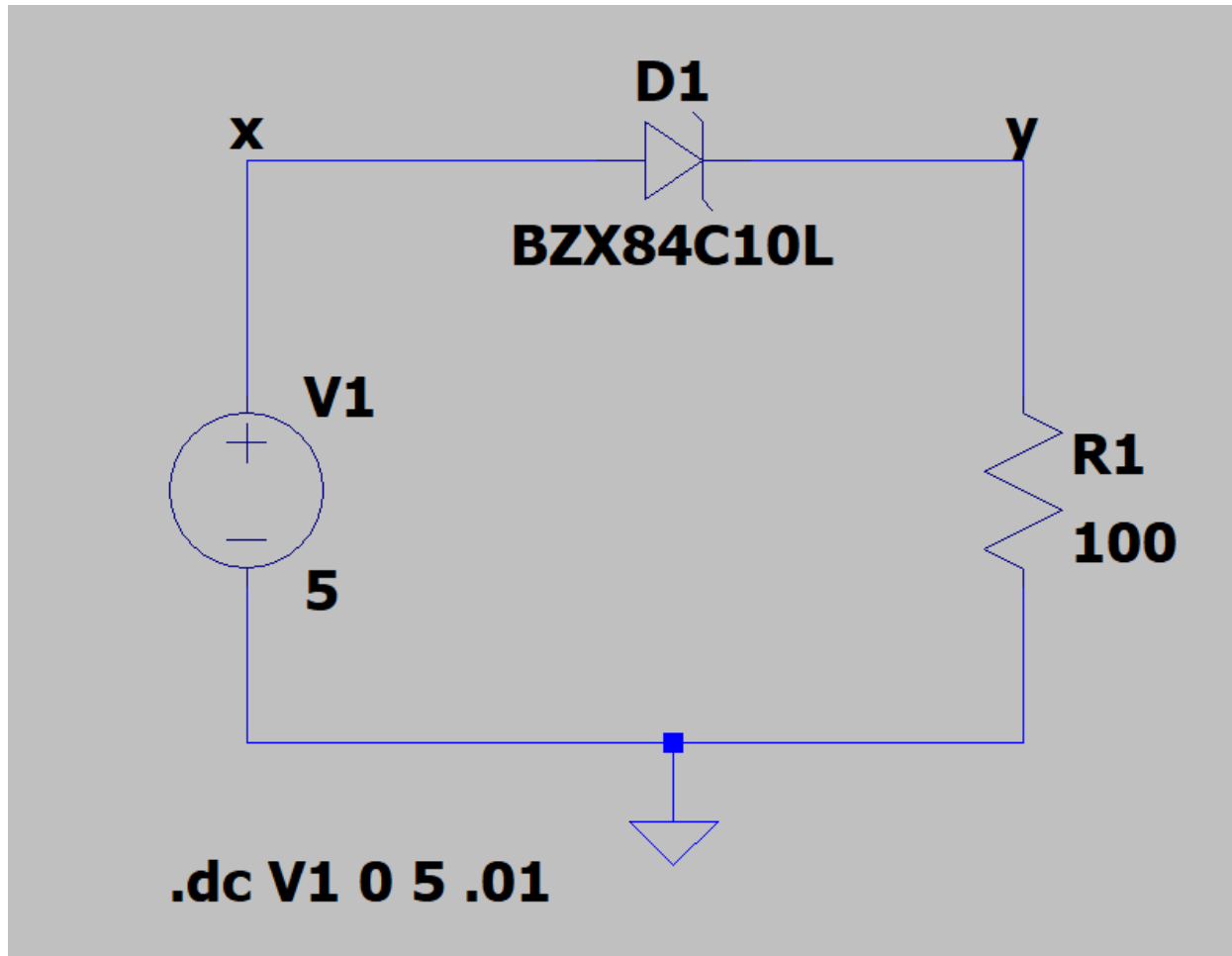

The model of Zener diode, I used here is BZX84C10L which has breakdown voltage of 10volts.

Output from LTspice simulation

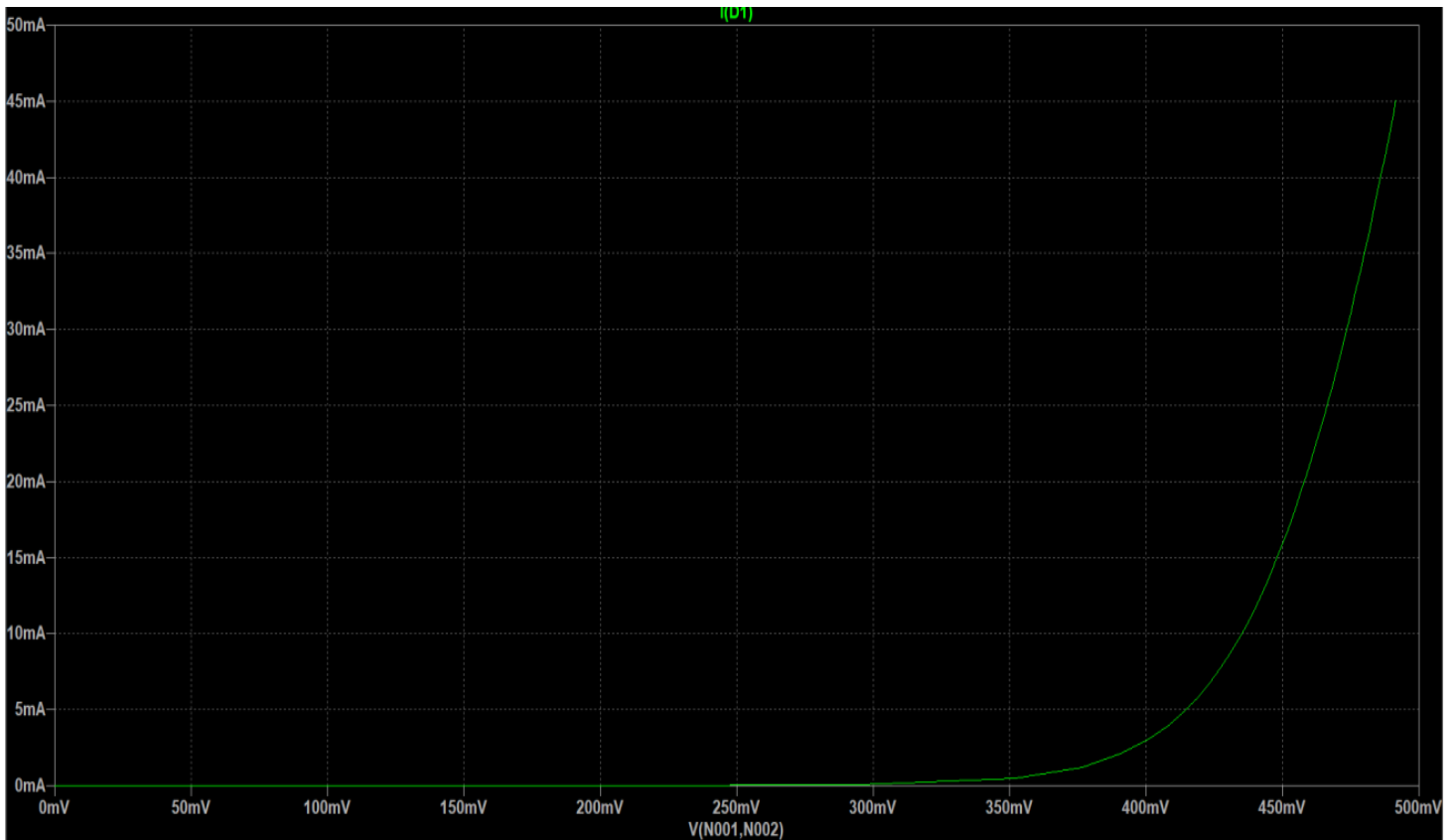


Observation Table:

| | | | | | | | |
|----|---|--|--|--|------------------------------|--|--|
| 16 | Characteristics of Zener diode Forward Bias | | | | | | |
| 17 | | | | | | | |
| 18 | Voltage across Zener diode VD(volts) | | | | Diode Forward current ID(mA) | | |
| 19 | 0 | | | | 0 | | |
| 20 | 0.15 | | | | 0.00069 | | |
| 21 | 0.2 | | | | 0.00143 | | |
| 22 | 0.25 | | | | 0.028 | | |
| 23 | 0.3 | | | | 0.092 | | |
| 24 | 0.35 | | | | 0.467 | | |
| 25 | 0.4 | | | | 2.955 | | |
| 26 | 0.45 | | | | 15.88 | | |
| 27 | 0.473 | | | | 30.078 | | |
| 28 | 0.48 | | | | 35 | | |


- LED(Light emitting Diode)

Circuit Diagram

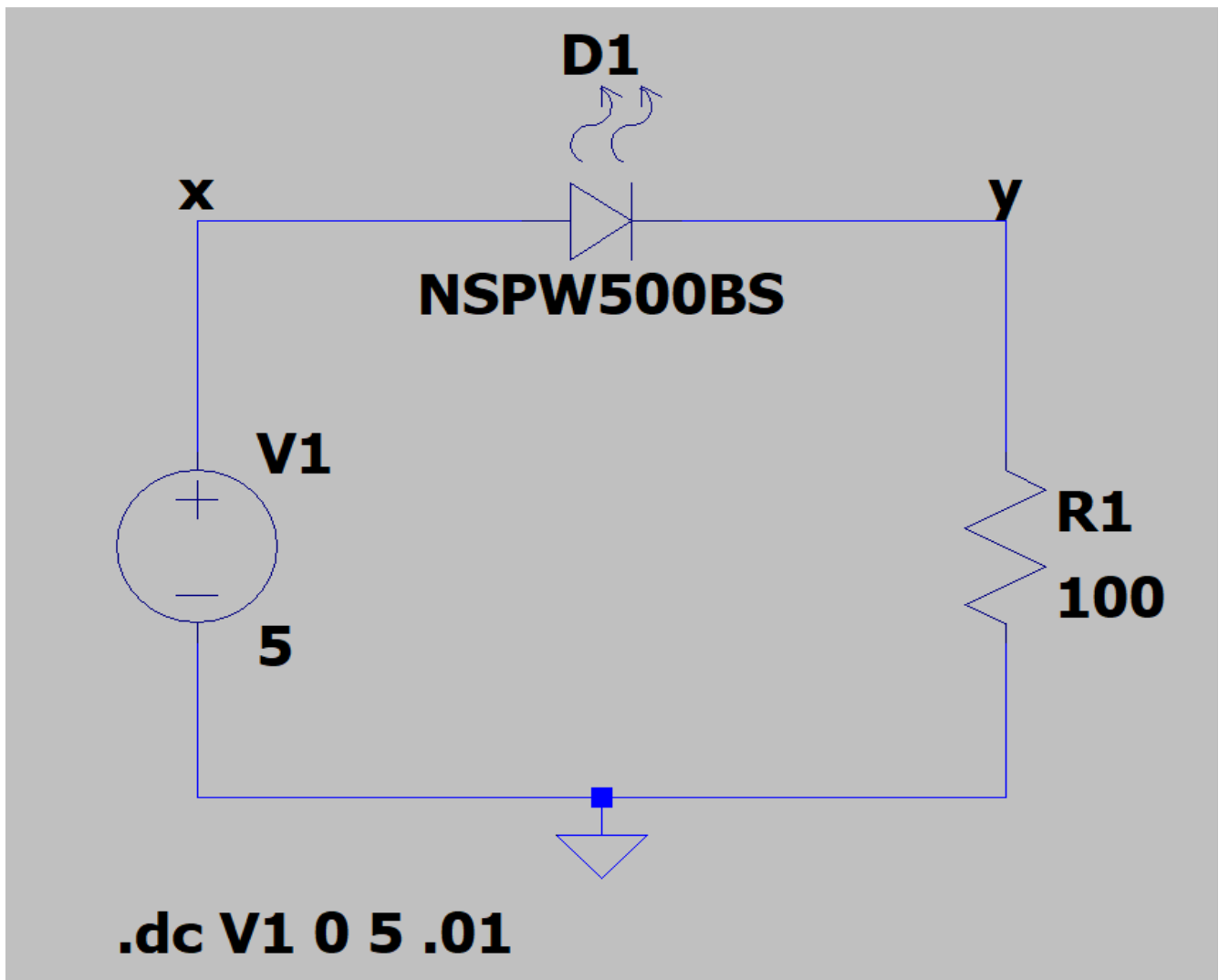

The model of LED, I used here is NSPW500BS which has breakdown voltage of 5volts.

Output from LTspice simulation

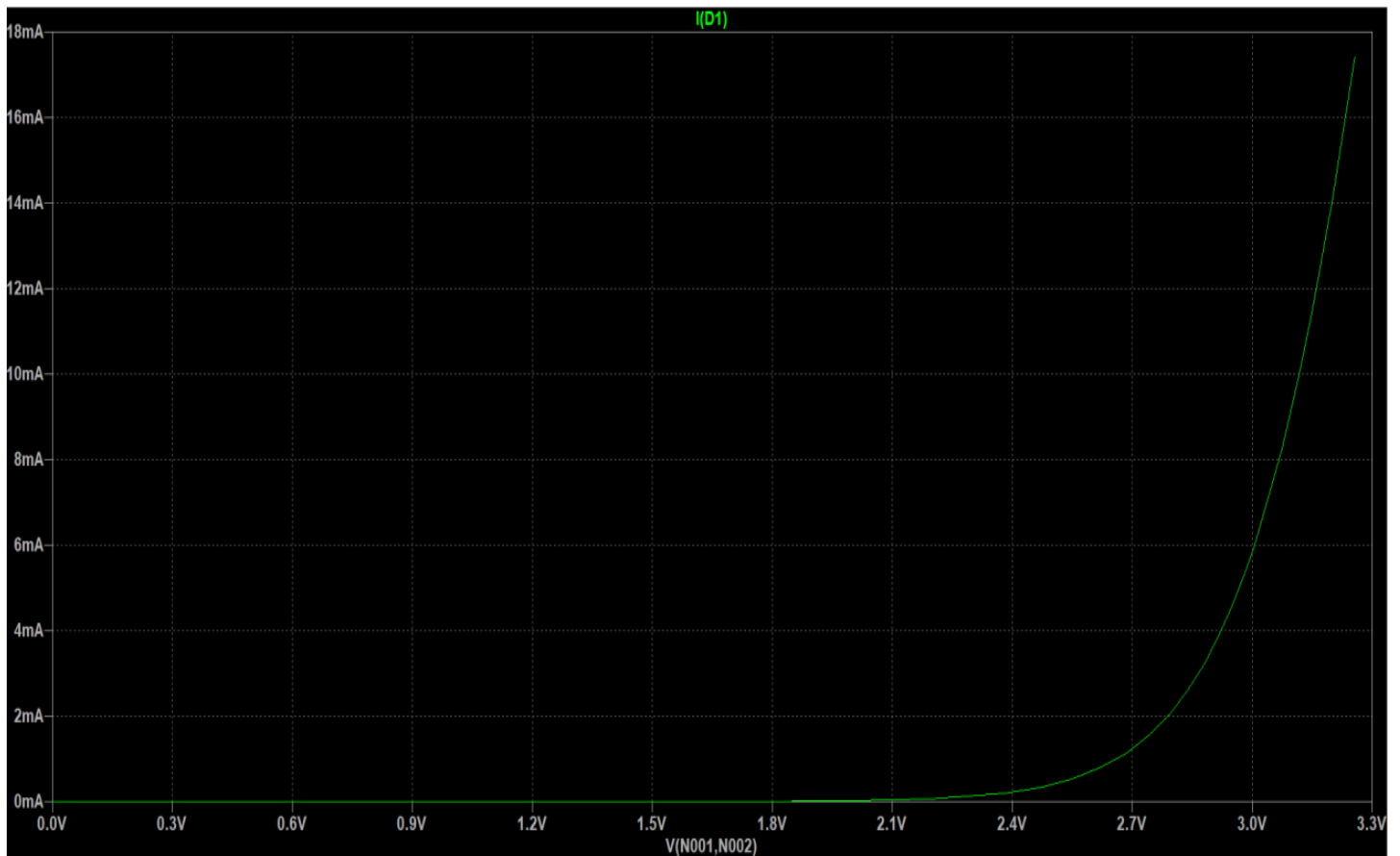

Observation Table:

| | | | | | |
|----|----------------------------------|--|--|--------------------------------|--|
| 33 | Characteristics of LED | | | | |
| 34 | | | | | |
| 35 | Voltage across LED V_D (volts) | | | LED Forward current I_D (mA) | |
| 36 | 0 | | | 0 | |
| 37 | 0.9 | | | 0.000045 | |
| 38 | 1.2 | | | 0.00025 | |
| 39 | 1.5 | | | 0.0013 | |
| 40 | 1.8 | | | 0.007 | |
| 41 | 2.1 | | | 0.042 | |
| 42 | 2.4 | | | 0.237 | |
| 43 | 2.7 | | | 1.255 | |
| 44 | 3 | | | 5.88 | |
| 45 | 3.12 | | | 10 | |
| 46 | 3.2 | | | 14.01 | |
| 47 | 3.23 | | | 16.31 | |

Results and Interpretation:

Forward Resistance = $r_{on} = dV_D/dI_D = 1/m$

$\ln I_D = (V_D/\eta V_T) + \ln I_s$ (I_s is the saturation current)

$V_T = 26\text{mV}$.


■ Silicon Diode

$I_D = 30.77\text{ mA}$ $V_D = 756.923\text{ mV}$

Slope 'm' at the above mentioned point is 0.481.

$r_{on} = 2.079\text{ ohms}$.

$\ln I_D$ v/s V_D plot

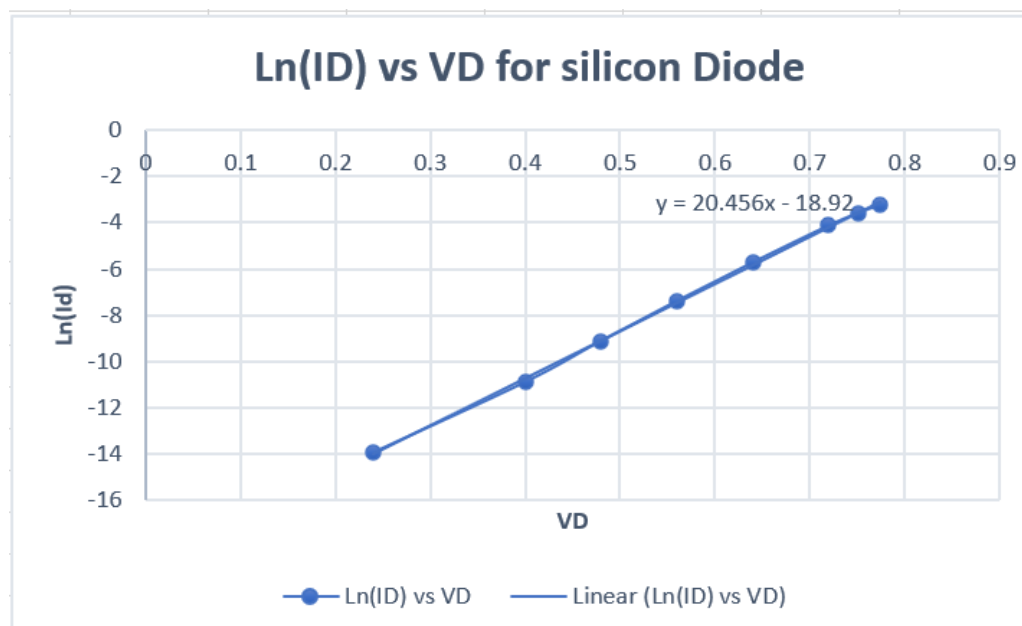

From the graph $1/\eta V_T = 20.456$

Therefore $\eta = 1.88$.

And $I_s = e^{-18.92}$


■ Zenor Diode

$$I_D = 30.77 \text{ mA} \quad V_D = 756.923 \text{ mV}$$

Slope 'm' at the above mentioned point is 0.791.

$$r_{on} = 1.26 \text{ ohms.}$$

$\ln I_D$ v/s V_D plot

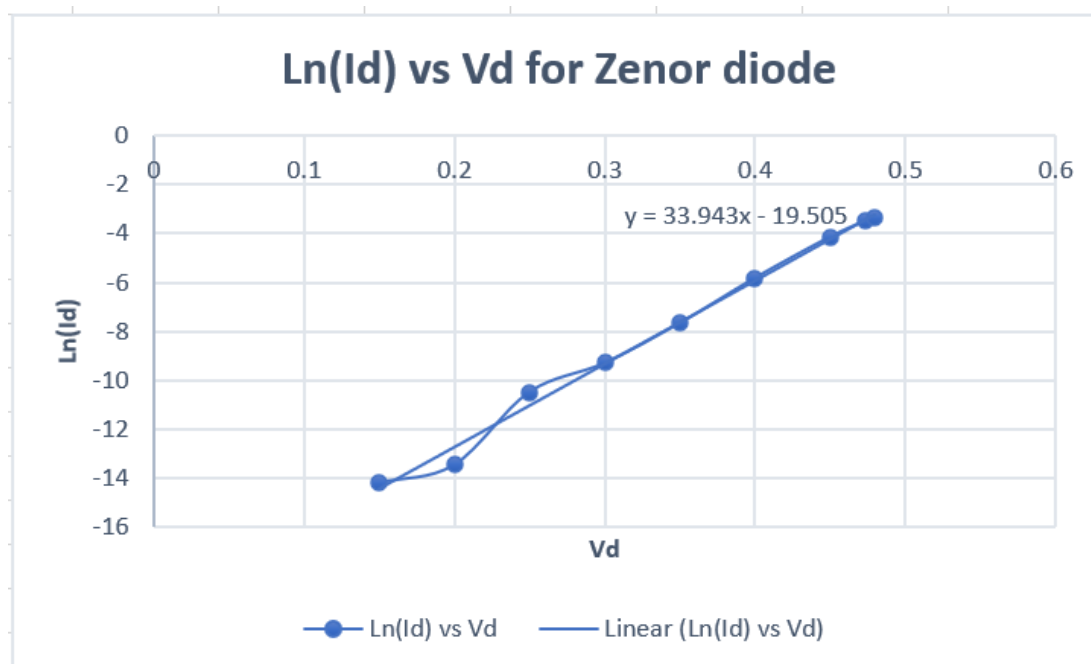

From the graph $1/\eta V_T = 33.943$

Therefore $\eta = 1.133$.

And $I_s = e^{-19.505}$


■ LED (light emitting diode)

$$I_D = 30.77 \text{ mA} \quad V_D = 756.923 \text{ mV}$$

Slope 'm' at the above mentioned point is 0.791.

$$r_{on} = 1.26 \text{ ohms.}$$

Ln I_D v/s V_D plot

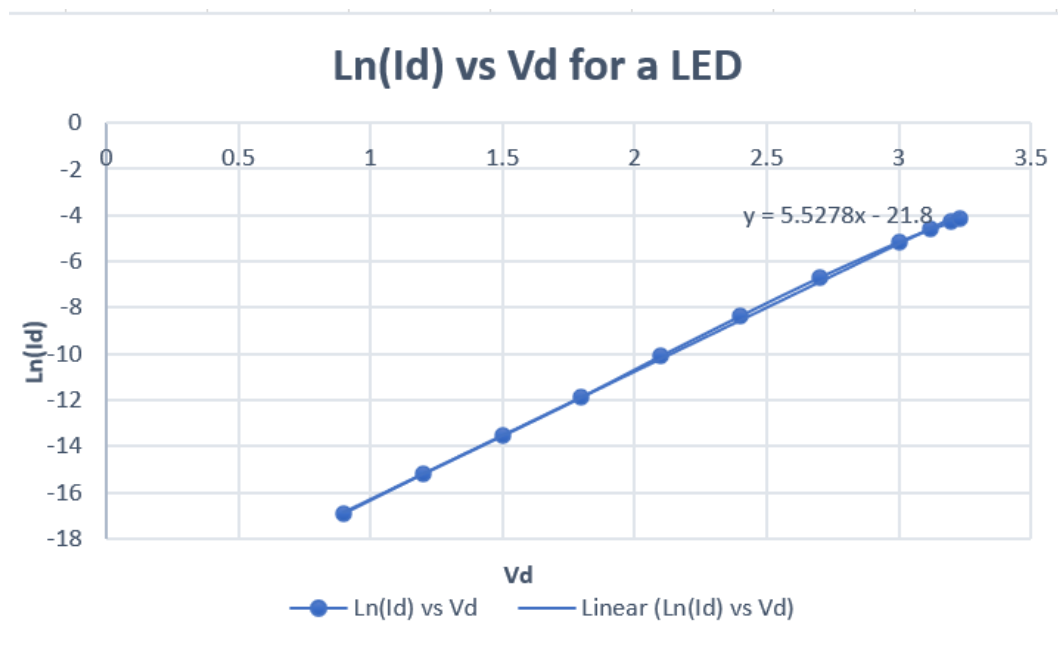

From the graph $1/\eta V_T = 5.5728$


Therefore $\eta = 6.9956$.

$$\text{And } I_s = e^{-21.8}$$

Part 2


Analyzing Reverse characteristics of 4.7V Zener diode

Circuit Diagram

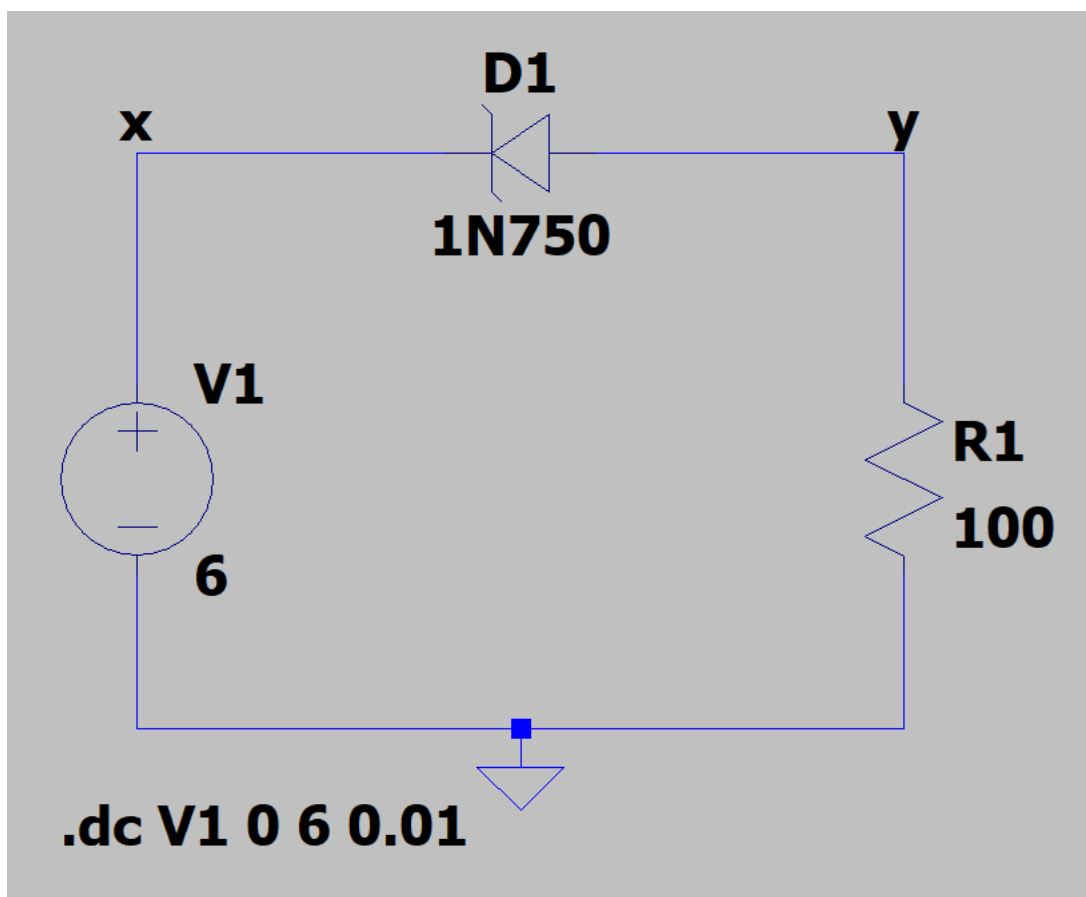

The model of Zener diode, I used here is 1N750 which has breakdown voltage of 4.7volts.

Output from LTspice simulation

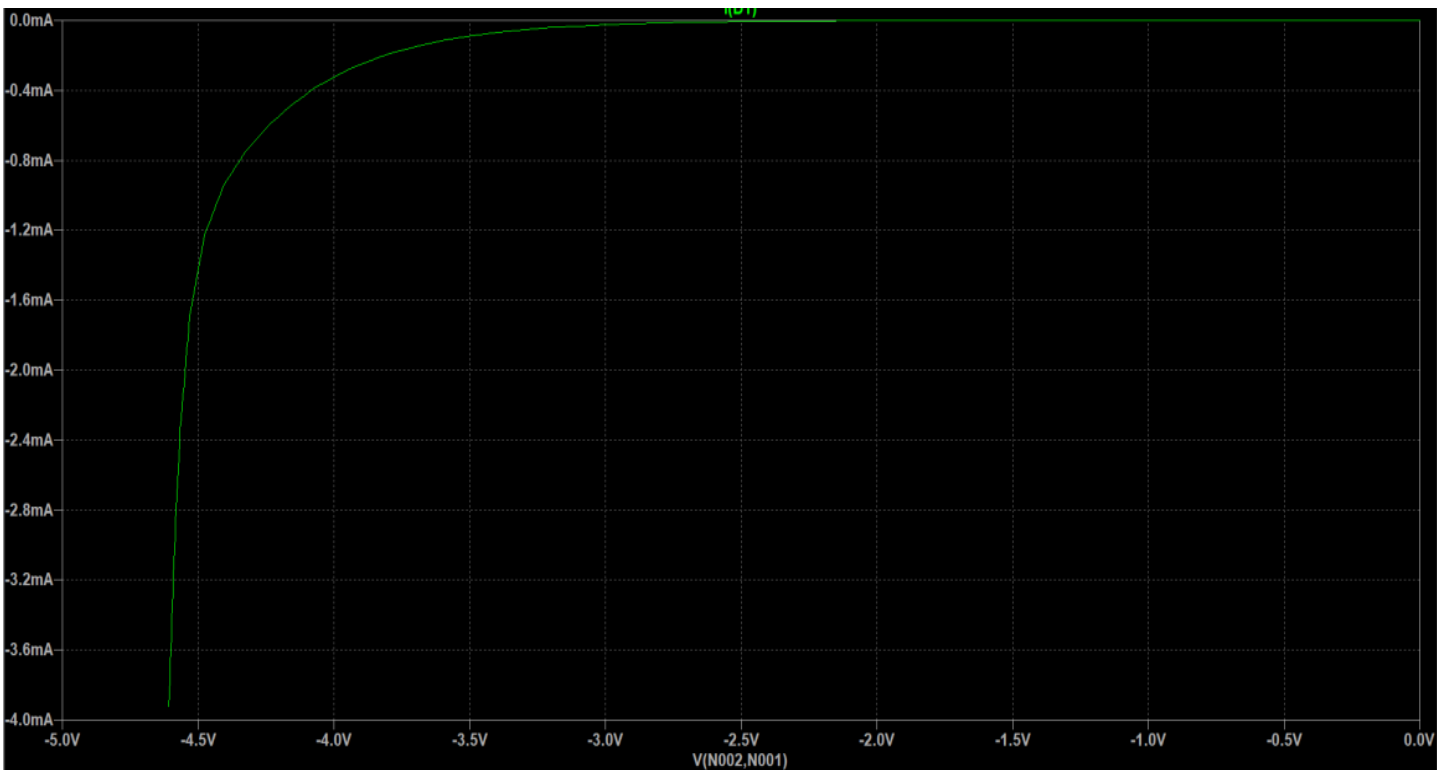

Observation Table:

| Characteristics of Zenor Diode Reverse Bias | | | | |
|---|--|--|------------------------------|--|
| Diode Reverse voltage VR(volts) | | | Diode Reverse Current IR(mA) | |
| 0 | | | 0 | |
| -1.495 | | | -0.0005 | |
| -2 | | | -0.00185 | |
| -2.5 | | | -0.00672 | |
| -3 | | | -0.024 | |
| -3.5 | | | -0.088 | |
| -4 | | | -0.324 | |
| -4.35 | | | -0.8 | |
| -4.47 | | | -1.2 | |
| -4.58 | | | -3.21 | |
| | | | | |

Results:

From the LTspice simulation graph the cutoff voltage of the Zener diode is approximately around -4.65 V.

Discussion:

In the forward characteristics of the diodes used in the experiment are all non-linear. Semiconductor diodes are characterized by non-linear current–voltage characteristics as the current flowing through a forward-biased common silicon diode is limited by the ohmic resistance of the PN-junction. In each forward characteristic current is suddenly increased at a particular voltage difference across the diodes.

Conclusion:

Here we plotted the forward and reverse characteristics of various diodes. We found respective forward resistance and cutoff voltage of Zener diode. In all the graphs the current across the diode is increased suddenly at a particular voltage difference across the diode.

Generally, we don't use Breakdown voltage as a application but Zener diode is a special case. It behaves as normal diode in forward case.