



**Power Systems Laboratory**  
**(EE3P006)**

**EXPERIMENT-3**

***Shorya Sharma***  
***19EE01017***

### Aim of the Experiment:

Fault detection and R-X trajectory plot in Transmission Line for different types of faults.

### Parameters & Data:

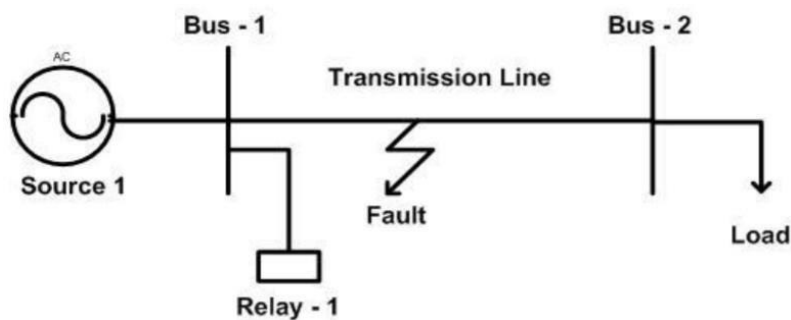


Fig. 1. Single-circuit transmission with source at one end and load at other end

- **Three Phase Source Parameter**

Phase to Phase voltage= 345 KV, Phase angle = 30-degree, Internal Connection  $Y_g$ , Short circuit level  $1500 \times 10^6$  VA, Base Voltage=400 KV, X/R ratio= 10, Frequency=50 HZ

- **Transmission Line Parameters**

No. of Phases=3, frequency=50HZ

Resistance per unit length  $[R_1, R_0] = [0.01537, 0.04612]$

Inductance per unit length  $[L_1, L_0] = [0.8858 \times 10^{-3}, 2.6547 \times 10^{-3}]$

Capacitance per unit length  $[C_1, C_0] = [13.06 \times 10^{-9}, 4.3551 \times 10^{-9}]$

Line length of each section = 200 Km

- **Load Data**


Load = 100 MW, 40 MVAR

## Apparent Impedance for Different Fault Types:


- 1) Three phase fault:  $Z = \frac{V_A}{I_A} \text{ or } \frac{V_B}{I_B} \text{ or } \frac{V_C}{I_C}$
- 2) Line to Line and Double Line to ground fault:  $Z = \frac{V_A - V_B}{I_A - I_B}$  (for AB or AB-to-ground fault)  
 $\frac{V_B - V_C}{I_B - I_C}$  (For BC or BC-to-ground fault)  
 $\frac{V_C - V_A}{I_C - I_A}$  (For CA or CA-to-ground fault)
- 3) Line to ground fault:  $Z = \frac{V_A}{I_A + kI_0}$  (For A phase-to-ground fault),  
 $\frac{V_B}{I_B + kI_0}$  (For B phase-to-ground fault),  
 $\frac{V_C}{I_C + kI_0}$  (For C phase-to-ground fault) , where  $k = \frac{Z_0 - Z_1}{Z_1}$

## CIRCUIT DIAGRAM


### 1. L-G

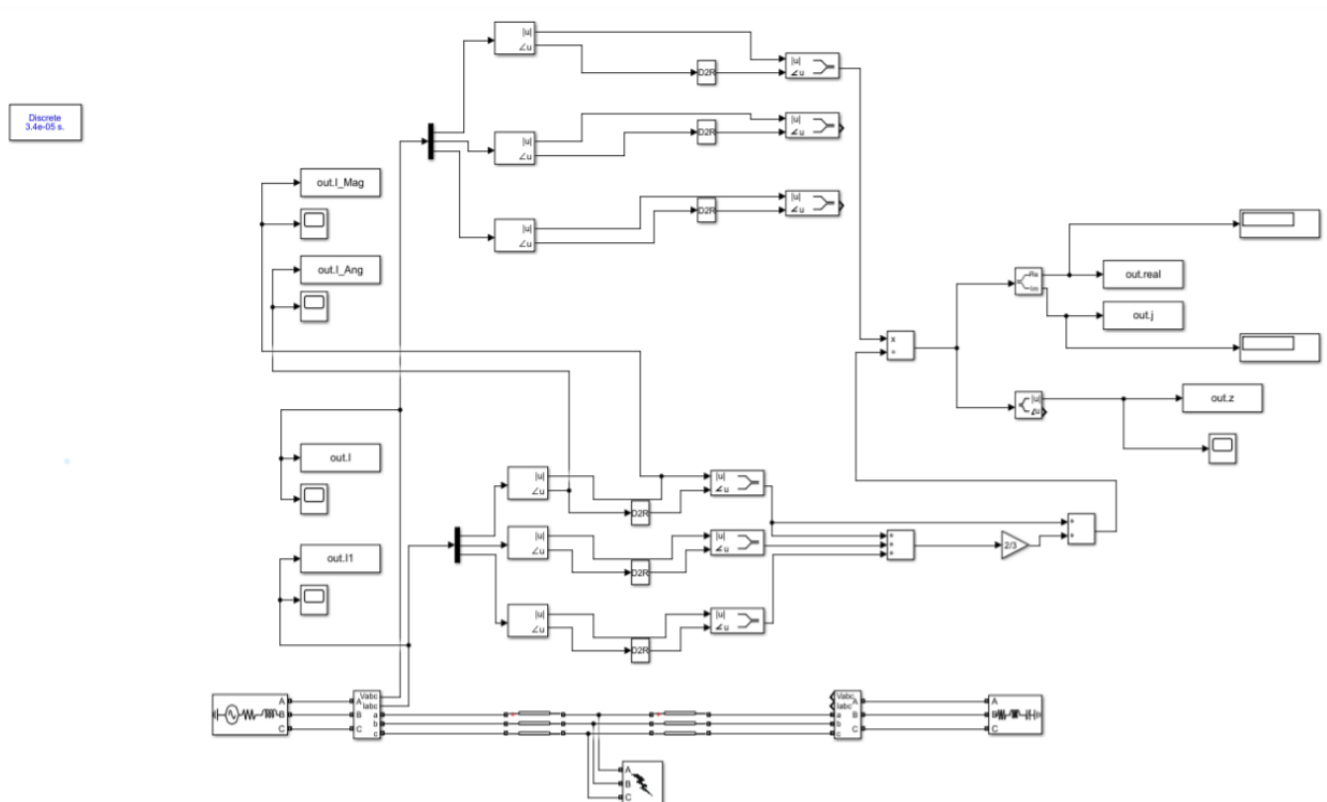

## 2. L-L & L-L-G

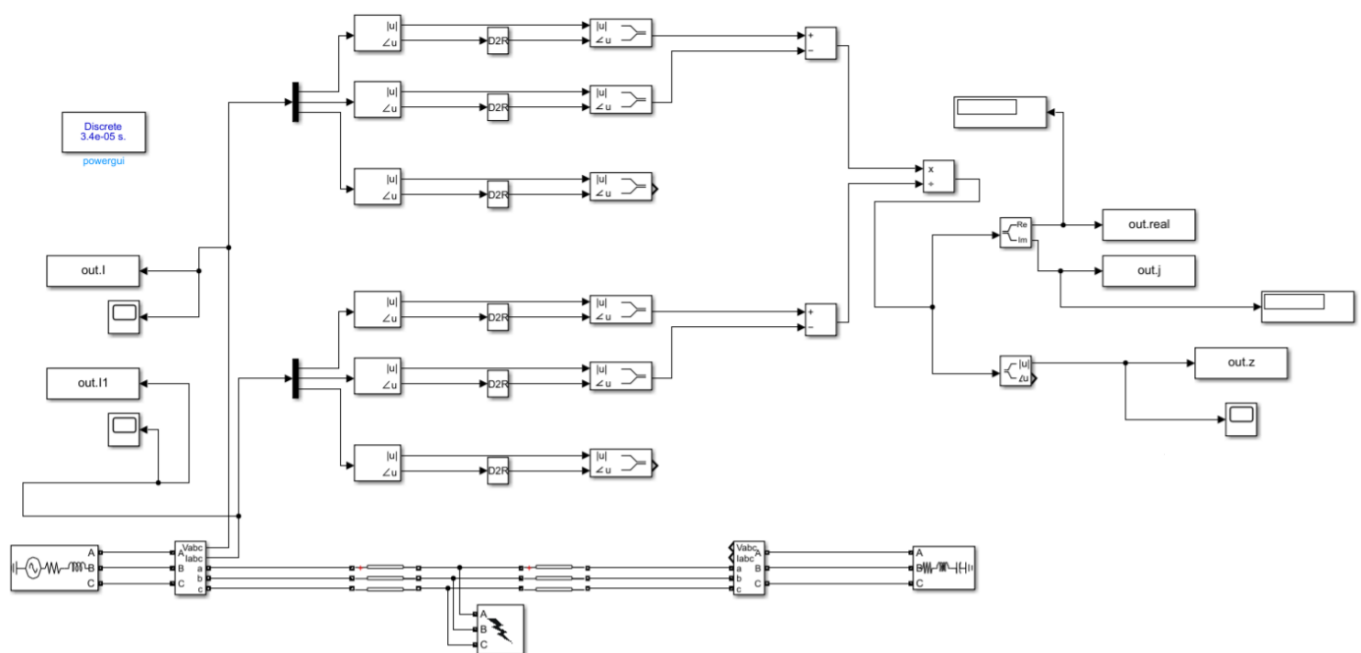

## 3. L-L-L

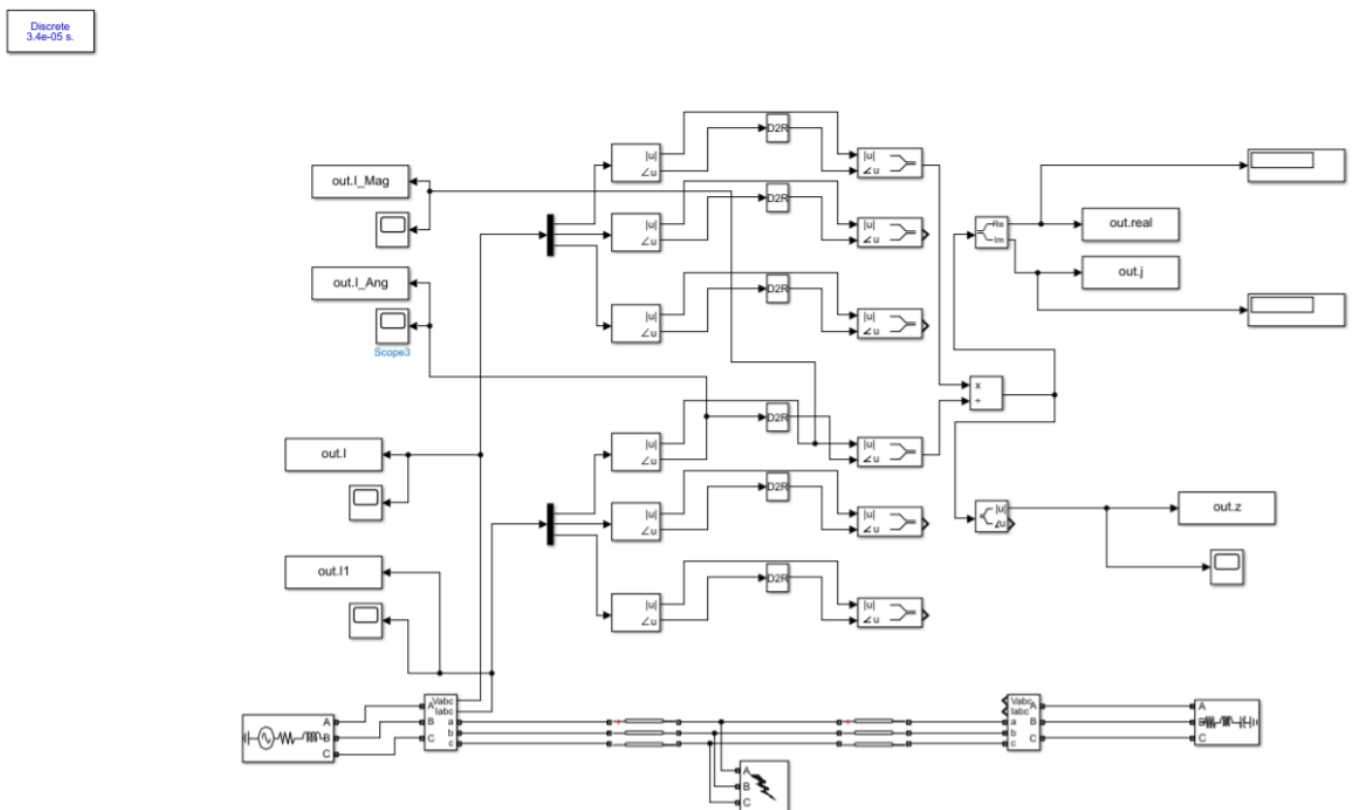


## Test Cases

- **Case-I:**


1. Create a single line to ground(A-G) fault at 50 Km from source- 1 with fault resistance of 0.1 Ohm at 0.7s

**(a) Plot the instantaneous current wave form**

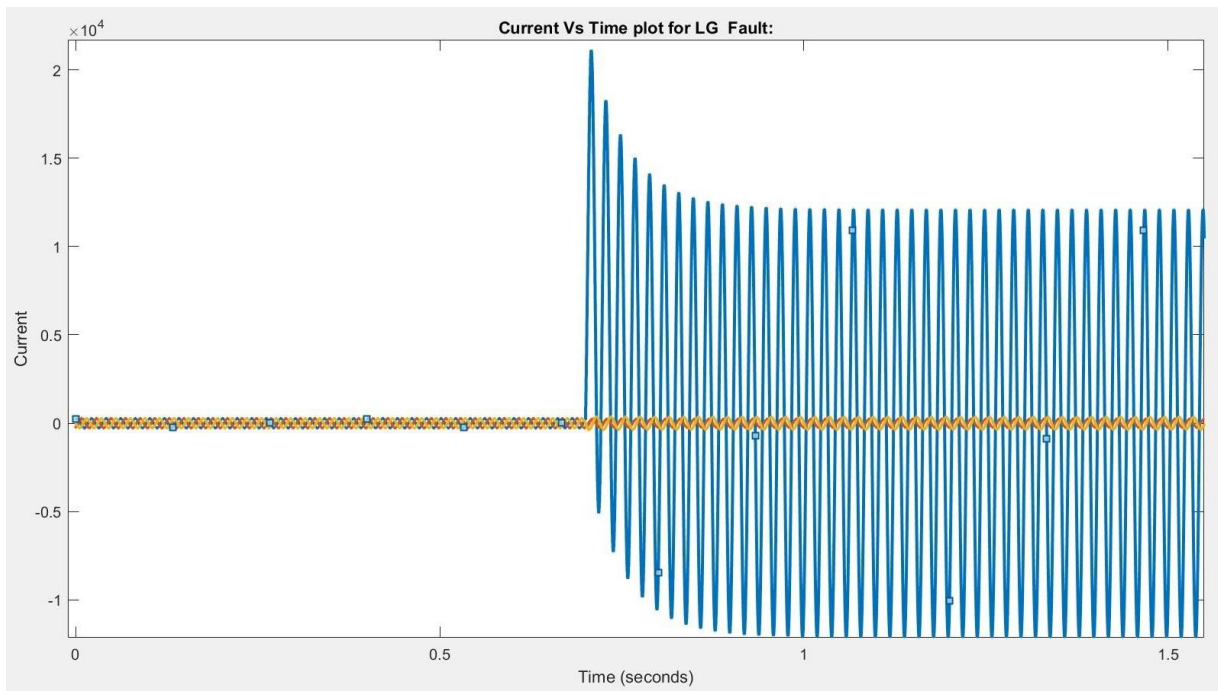

**Fig-1:** Plot the instantaneous current wave form of all the phases at bus B- 1 with single line to ground(A-G) fault at 50 Km from source- 1 with fault resistance of 0.1 Ohm at 0.7


**(b) Plot the instantaneous voltage waveform**

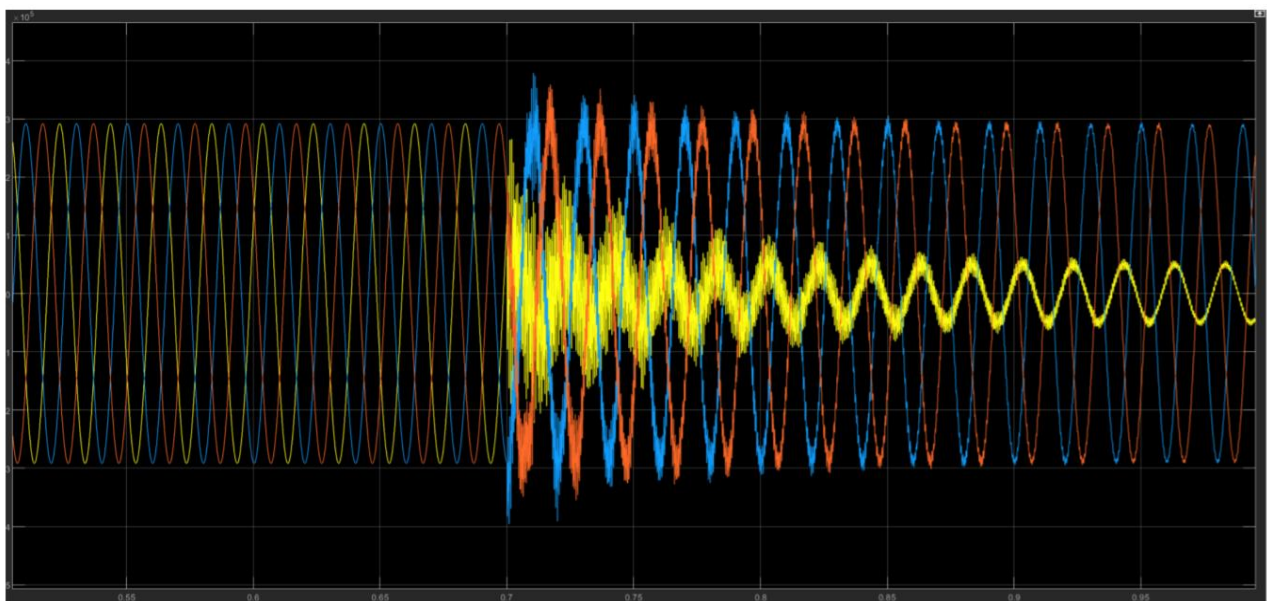


**Fig-2:** Plot the instantaneous voltage wave form of all the phases at bus B- 1 with single line to ground(A-G) fault at 50 Km from source- 1 with fault resistance of 0.1 Ohm at 0.7 second

(c) Plot Magnitude and phase angle of fundamental current of phase-A w.r.t time using Fourier Block in Simulink.


Magnitude:

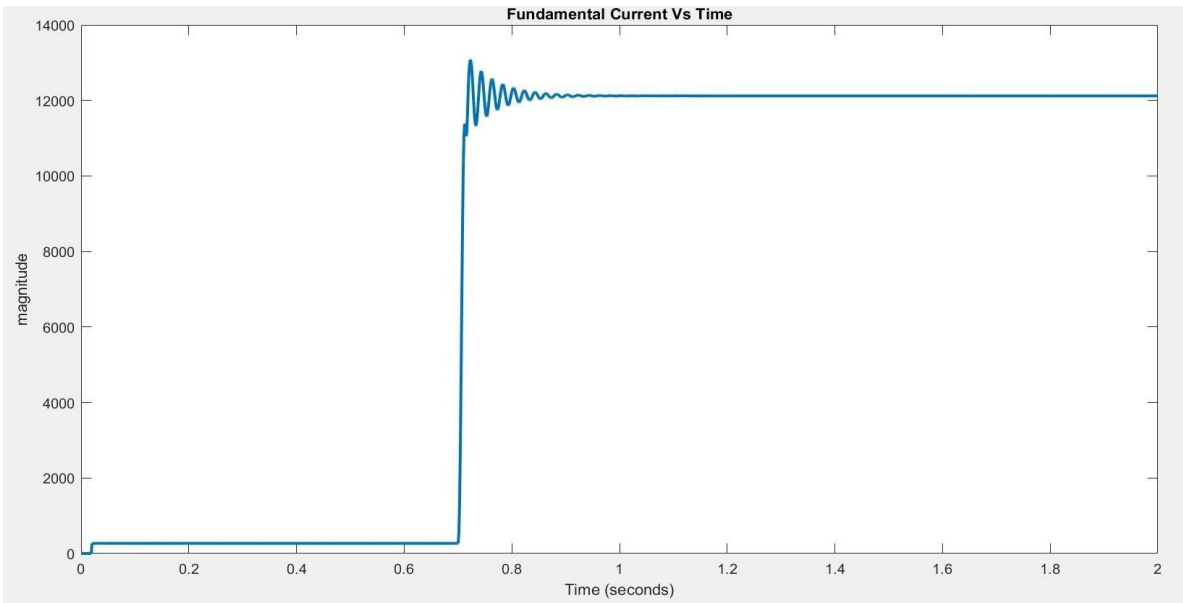


Phase:

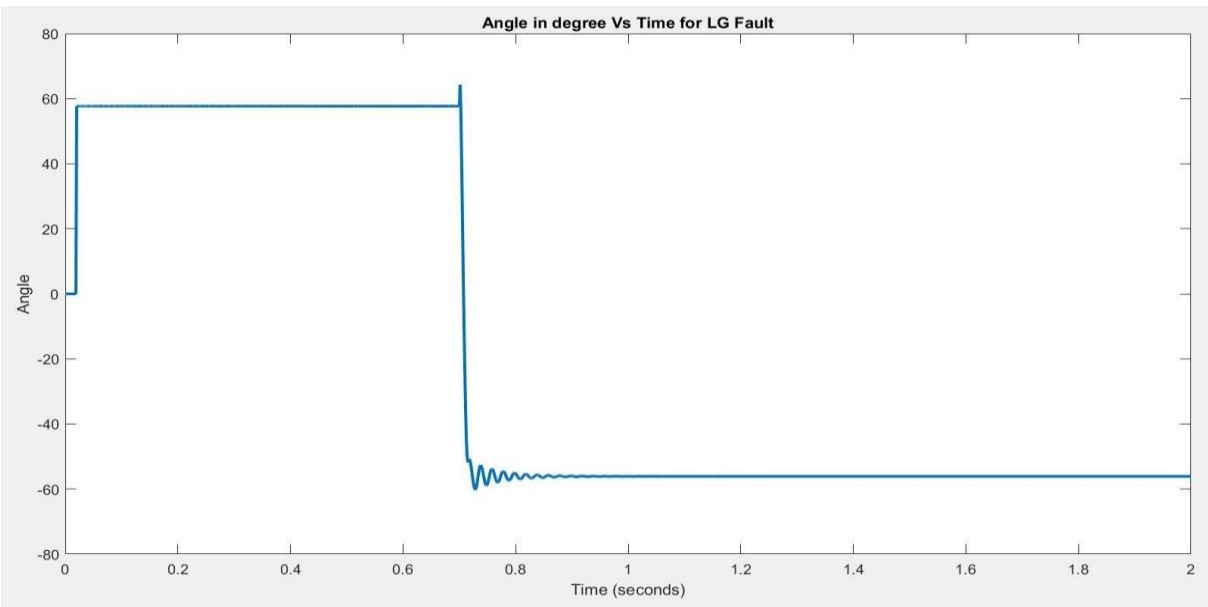

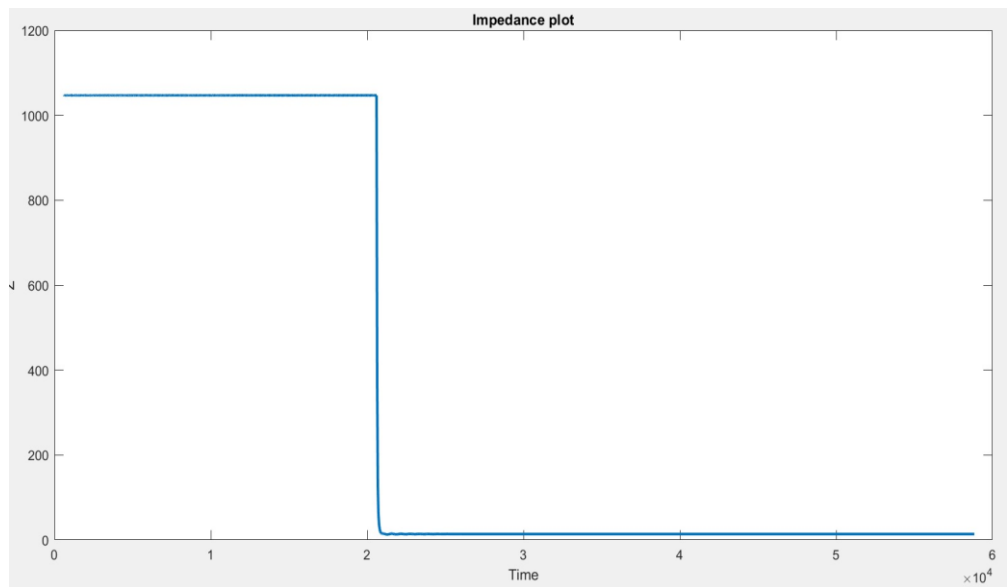**(d) Plot the Impedance plot (Z Versus time). (Fault resistance = 0.1Ω)**




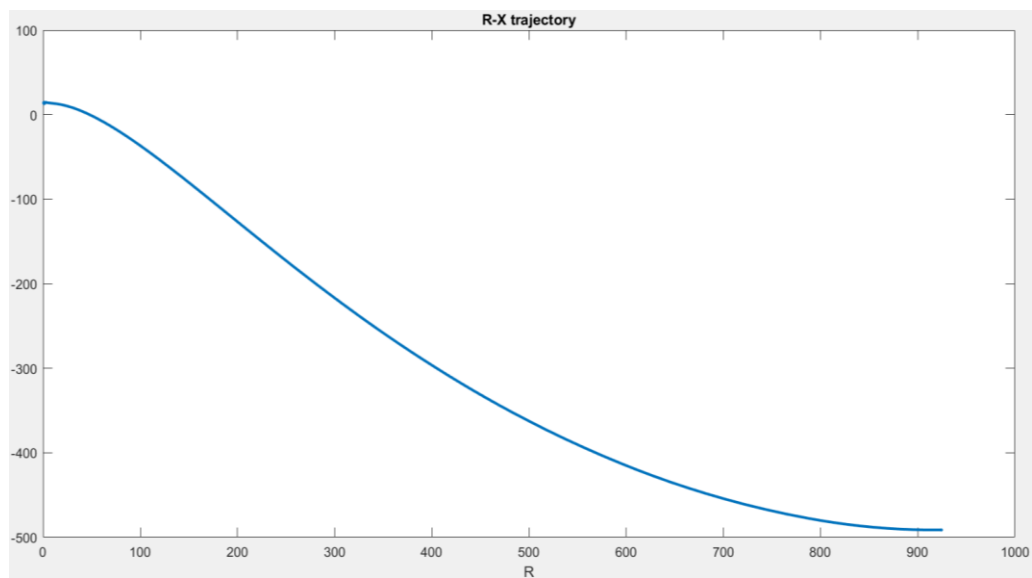**(e) Plot the R-X trajectory (Resistance Versus Reactance). (Fault resistance = 0.1Ω)**




## 2. L-L (A-B) fault (L-L impedance = $0.1\Omega$ ) (Fault resistance = $0.1\Omega$ )

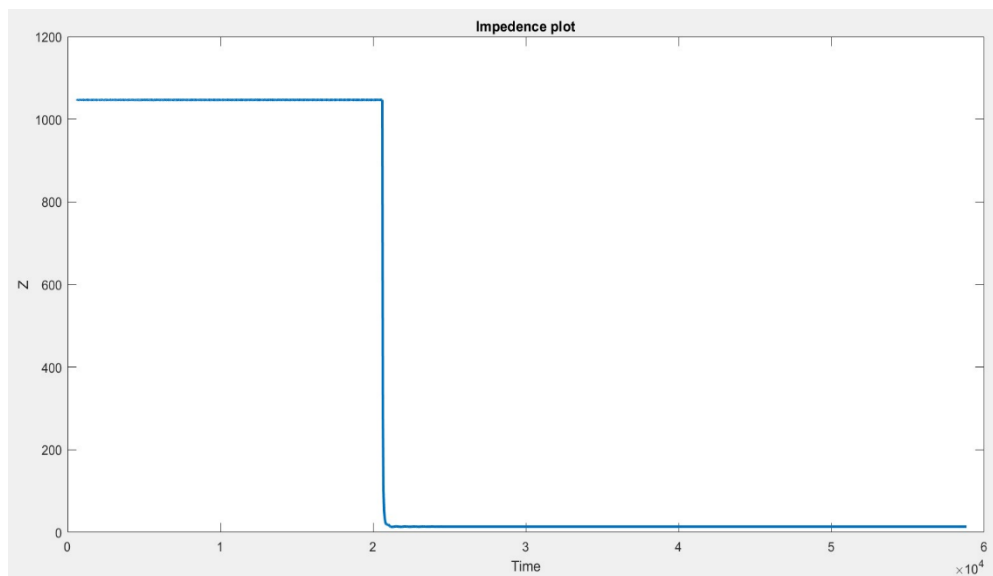**Plot the Impedance plot (Z Versus time)**



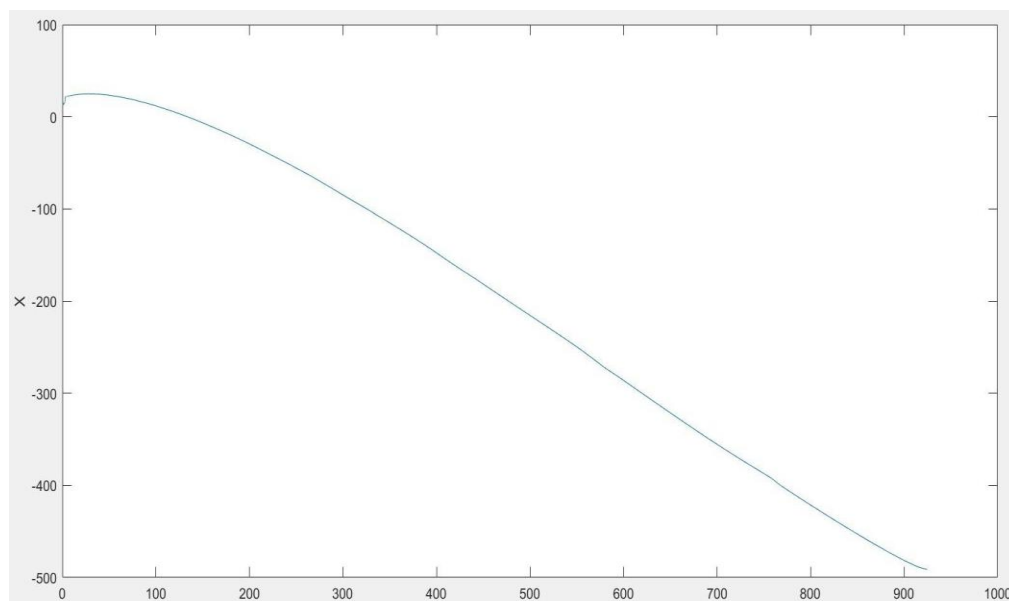
**plot of R-X trajectory (Resistance Versus Reactance). (Fault resistance =  $0.1\Omega$ )**






3. L-L-G (A-B-G) fault. (Fault resistance =  $0.1\Omega$ ) (Fault resistance =  $0.1\Omega$ )


Plot the Impedance plot (Z Versus time)

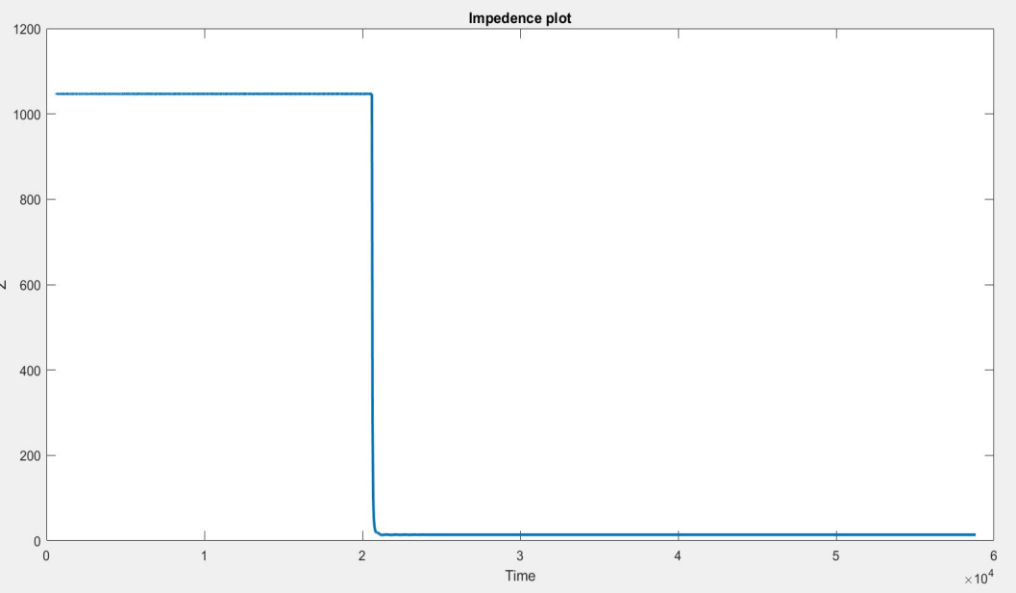

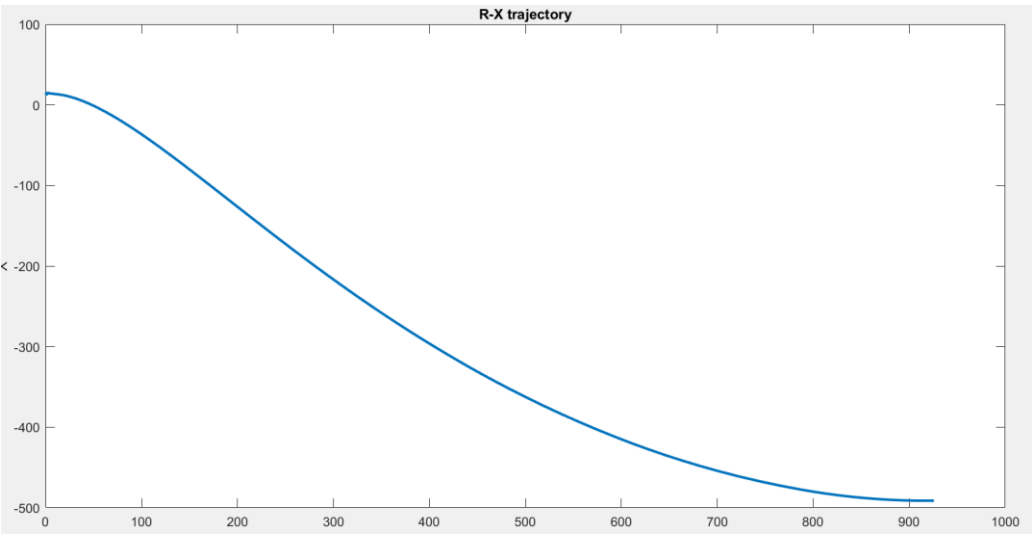
plot R-X trajectory (Resistance Versus Reactance).



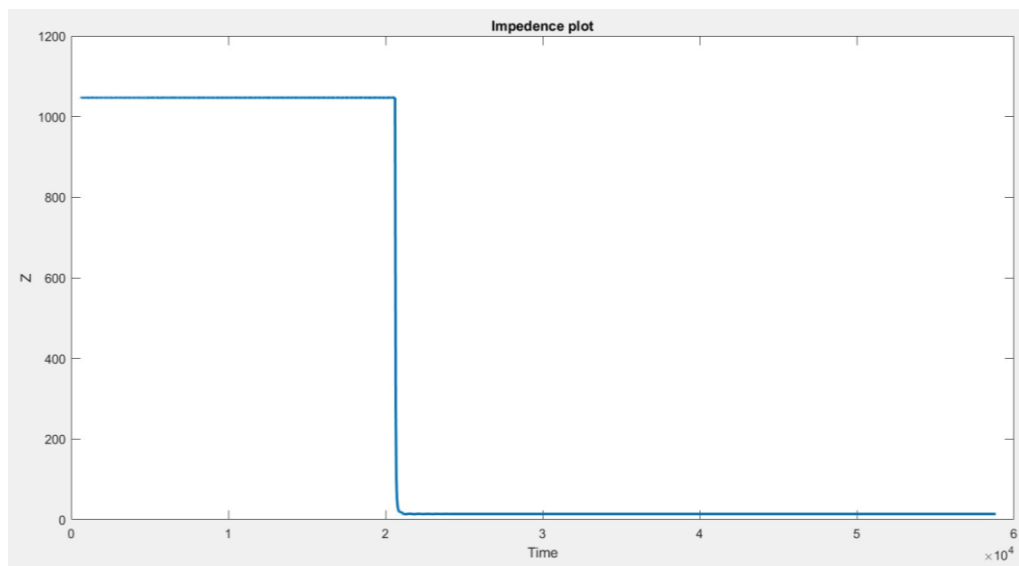**4. L-L-L (A-B-C) fault. (Fault resistance = 0.1) Plot the Impedance plot (Z Vs time)**




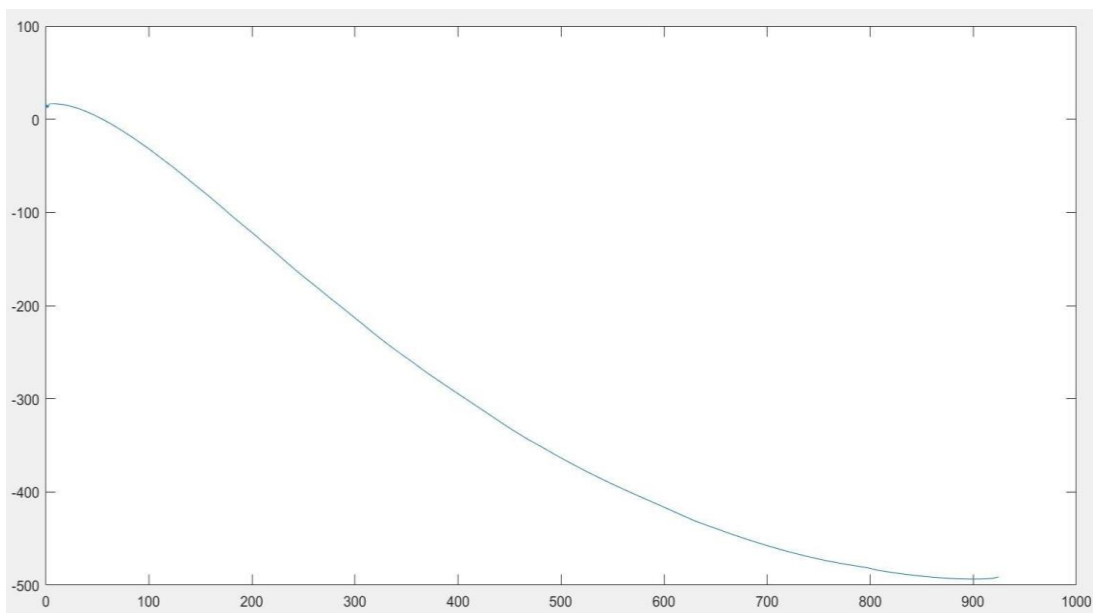**R-X trajectory (Resistance Versus Reactance).**




## **Case – II:**

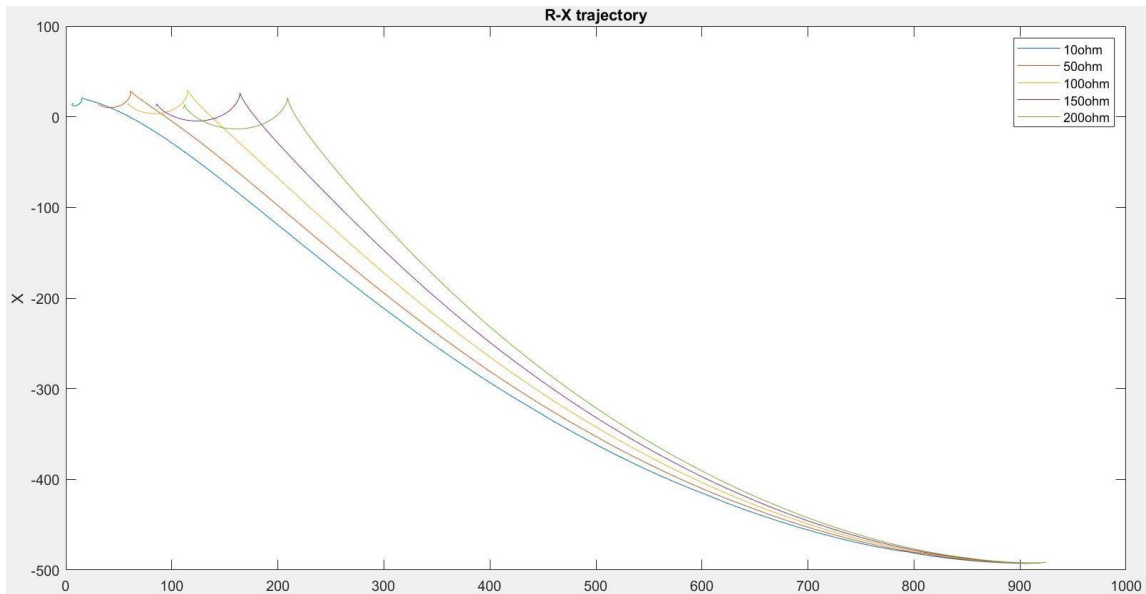
**Impact of fault resistance on R-X trajectory.  $R_f = 10, 50, 100, 150, 200$  (In ohms). for L-G fault. (Fault at 50 Km from source- 1)**



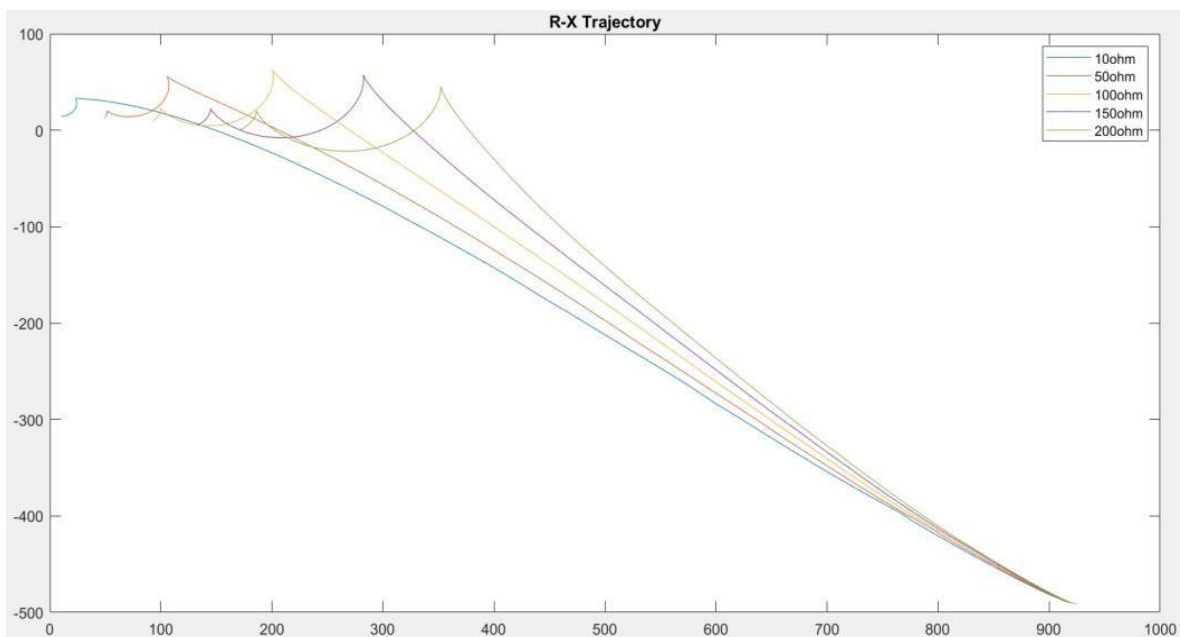
**For L-L fault. (Fault at 50 Km from source- 1),  $R(L-L) = 10, 50, 100, 150, 200$ (In ohms).**



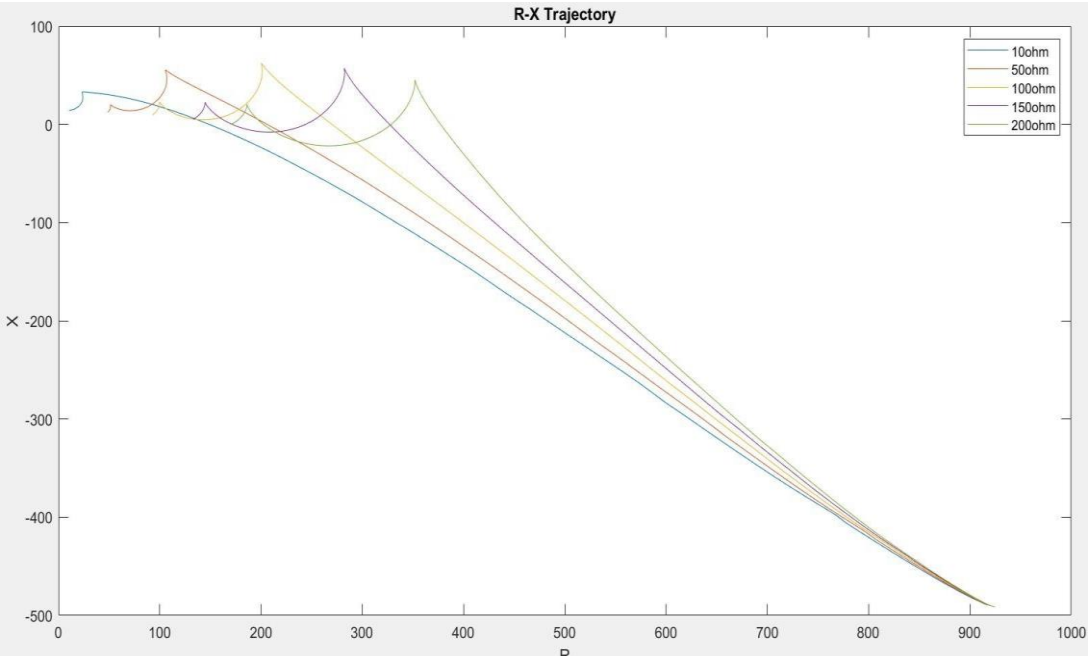**For L-L-G fault. (Fault at 50 Km from source- 1),  $R(L-L) = R(L-G)$  10, 50, 100, 150, 200 (In ohms).**



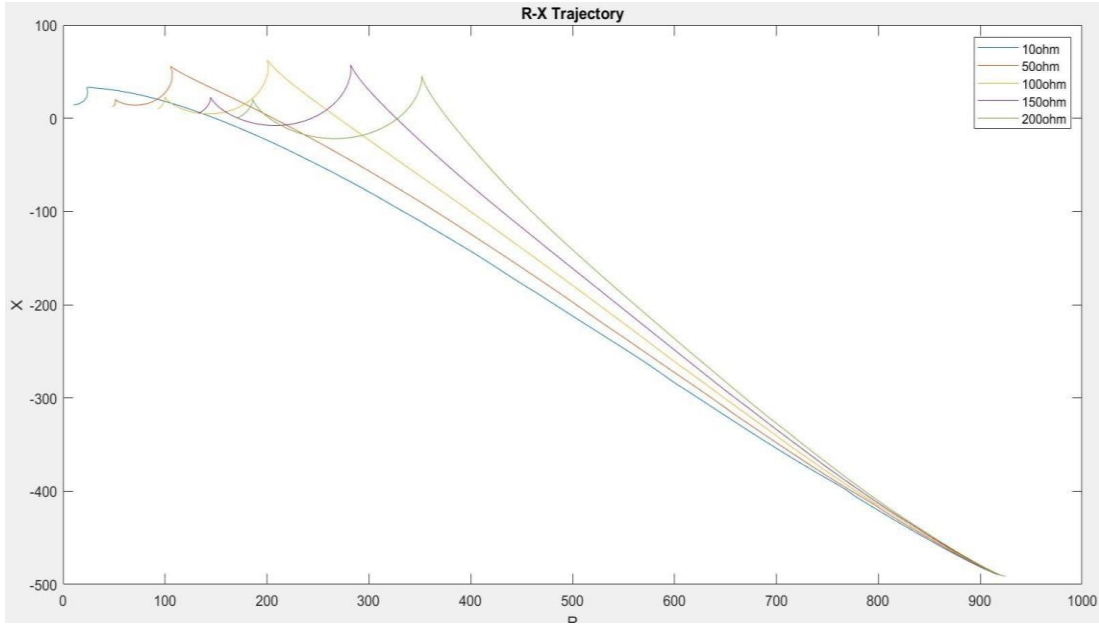**For L-L-L fault. (Fault at 50 Km from source- 1),  $R(L-L-L)$  10, 50, 100, 150, 200(In ohms).**




### Case-III:

Types of fault	Fault Resistance( $\Omega$ )							
	10		50		100		200	
	R	X	R	X	R	X	R	X
No Fault	924.3	-491.3	924.3	-491.3	924.3	-491.3	924.3	-491.3
L-G	6.718	13.95	30.1	13.7	58.48	13.15	110.7	9.698
LL	6.718	13.95	30.1	13.7	58.48	13.15	110.7	9.698
LL-G	6.718	13.95	30.1	13.7	58.48	13.15	110.7	9.698
LLL	6.718	13.95	30.1	13.7	58.48	13.15	110.7	9.698
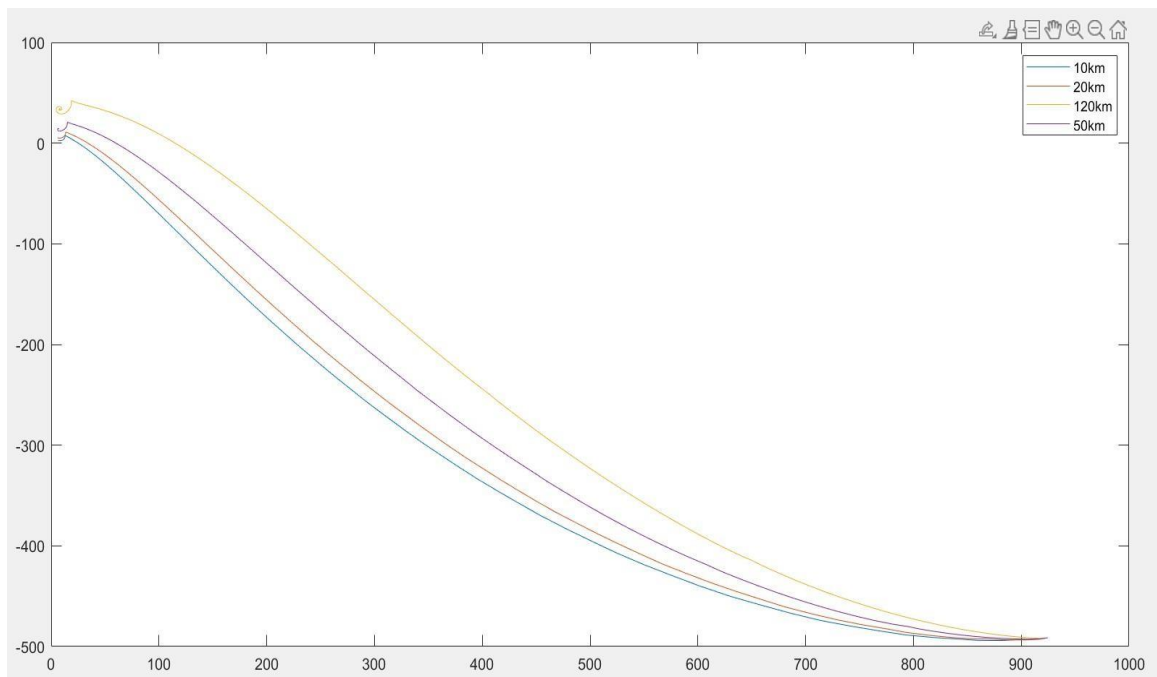
### Case-IV:


Impact of fault location on R-X trajectory. FL = 10, 20, 50, 120 (In km).

(Fault resistance =  $10\Omega$ ) plots for L-G




**R**


plots for L-L

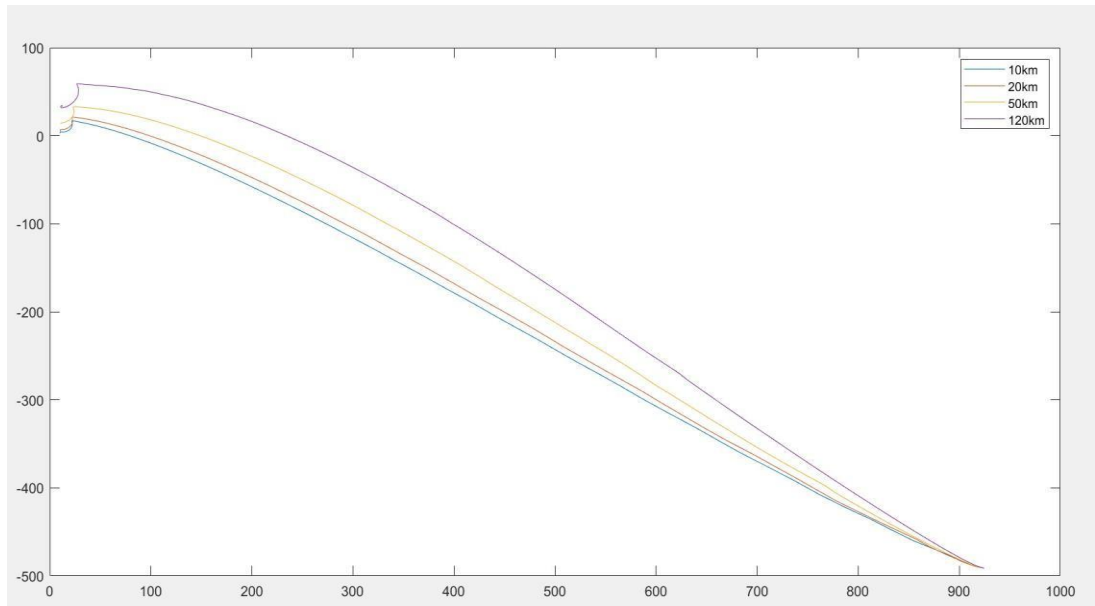

plots for L-L-G

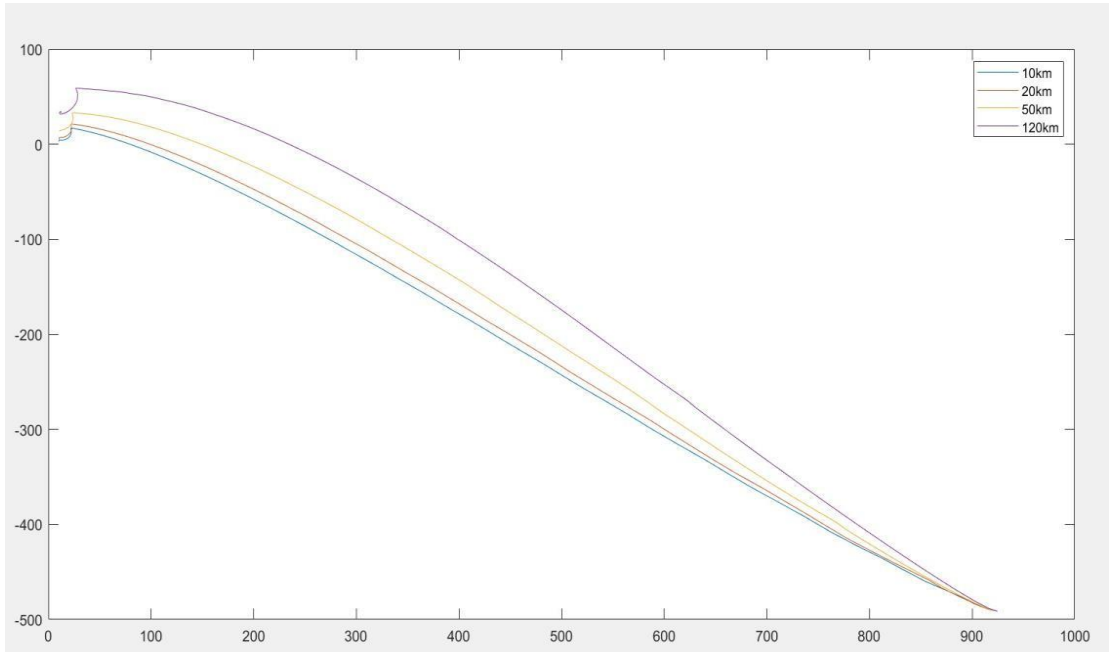

## plots for L-L-L

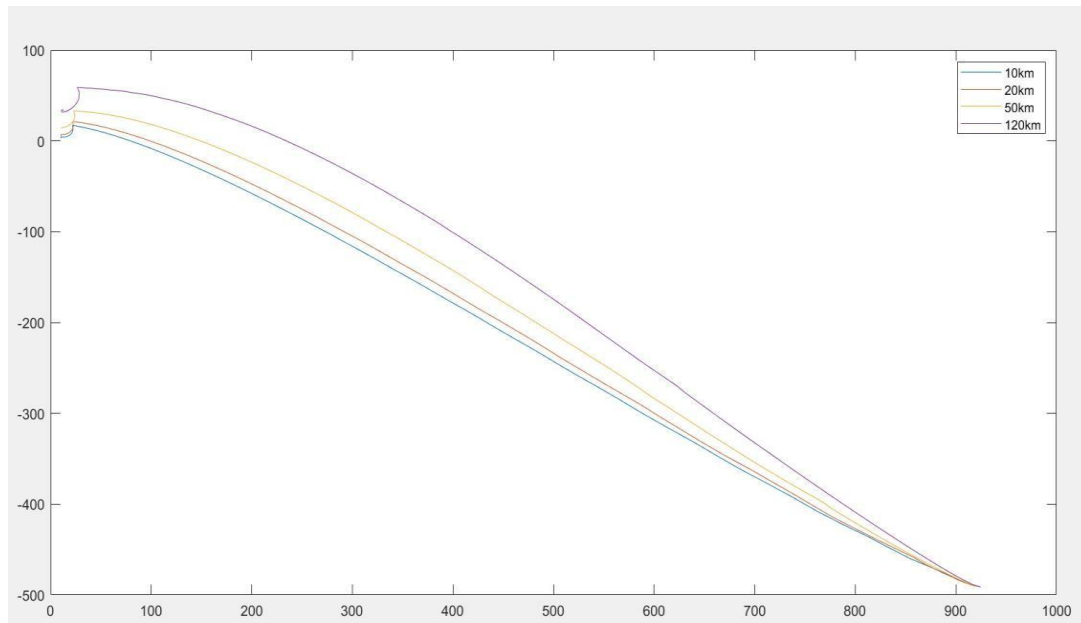

## Case-V:

Types of faults	Fault Location (KM)							
	10		20		50		120	
	R	X	R	X	R	X	R	X
No Fault	924.3	-491.3	924.3	-491.3	924.3	-491.3	924.3	-491.3
L-G	10.17	2.759	9.23	5.422	10.52	13.98	11.75	35.42
LL	10.17	2.759	9.23	5.422	10.52	13.98	11.75	35.42
LL-G	10.17	2.759	9.23	5.422	10.52	13.98	11.75	35.42
LLL	10.17	2.759	9.23	5.422	10.52	13.98	11.75	35.42

## Conclusion

From this experiment we have seen that impedance of the transmission line decreases and it depends upon how far the fault is from the source.